


Strain Measurements

2103-602

Measurement and
Instrumentations

Review of Stress and Strain

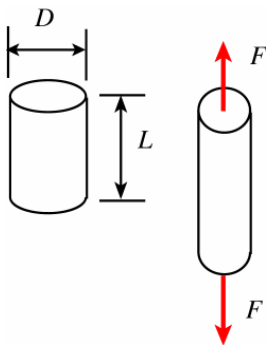Axial stress σ_a , axial strain ε_a , transverse strain ε_t , Poisson's ratio ν , and Young modulus E are






$$\sigma_a = \frac{F}{A} \quad \varepsilon_a = \frac{dL}{L} \quad \varepsilon_t = \frac{dD}{D}$$

$$\nu = \frac{-\varepsilon_t}{\varepsilon_a} = \frac{-dD/D}{dL/L} \approx 0.3$$

$$E = \frac{\sigma}{\varepsilon}$$

Electrical-Resistance Strain Gages

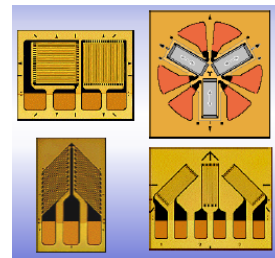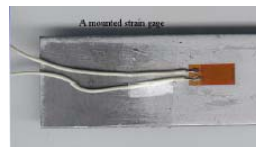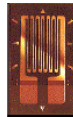- Widely used for strain measurement
- Resistance of gage material changes with deformation
- Use to measure local strain in axial direction of the gage
- Can measure various components of strain using rosette gages



Principle of Operation

Electrical resistance of any gage wire is determined by

$$R = \frac{\rho L}{A}$$

where L is the gage length

A is area of the wire

ρ is resistivity in $\Omega\text{-m}$

Note: - The strain increased, R increased

- R linearly increases with strain,
provided a constant temperature

Relation of R and ε

From $R = \frac{\rho L}{A}$ where $A = cD^2$

$c = 1$ (square) and $c = \pi/4$ (circular).

The change of R is then

$$\begin{aligned} dR &= d\left(\frac{\rho L}{A}\right) \\ &= \frac{L}{A}d\rho + \frac{\rho}{A}dL - \frac{\rho L}{A^2}dA \\ &= \frac{L}{A}d\rho + \frac{\rho}{A}dL - \frac{2\rho L}{A} \frac{dD}{D} \end{aligned}$$

or $\frac{dR}{R} = \frac{d\rho}{\rho} + \frac{dL}{L} - \frac{2dD}{D}$

$$\frac{dR/R}{dL/L} = \frac{dR/R}{\varepsilon_a} = \frac{d\rho/\rho}{\varepsilon_a} + 1 + 2\nu$$

If ρ is constant, i.e. resistivity does not change with strain, thus


$$\frac{dR/R}{\varepsilon_a} = 1 + 2\nu \equiv \text{Gage Factor (GF)}$$

Gage Factor

$$\frac{dR/R}{\varepsilon_a} = 1 + 2\nu \equiv \text{Gage Factor (GF)}$$

- GF or the sensitivity typically varies from 1.6 to 4
- Large GF (a large change in resistance for a given strain) is desirable
- R is normally 120Ω or 350Ω
- Axial strain ε_a is in the range of 10^{-6} to 10^{-3} , resulting in $dR = 0.00024$ - 0.24Ω .
- Note that how small dR is, so we cannot simply stick an ohm meter across the strain gages.
- Wheatstone bridges circuit are commonly used to amplify such low resistance values.

Wheatstone Bridge

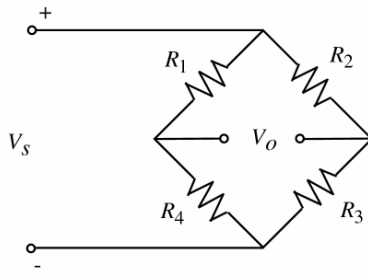


Output voltage V_o is

$$V_o = V_s \frac{R_3 R_1 - R_4 R_2}{(R_2 + R_3)(R_1 + R_4)}$$

If all four resistors are identical or if $R_3 R_1 = R_4 R_2$, the bridge is balanced, i.e. $V_o = 0$.

Quarter Bridge Circuit (one active gage)

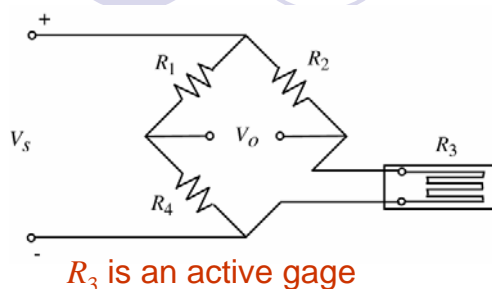

The bridge is initially balanced, when $R_{3i} R_1 = R_4 R_2$. Thus

$$V_{oi} = 0$$

If $R_1 = R_2 = R_{3i} = R_4$, then

the strain causes a change in R_3 as

$$R_{3i} + dR_3$$

The output voltage per input voltage is

$$\frac{V_o}{V_s} = \frac{(R_{3i} + dR_3)R_1 - R_4 R_2}{(R_2 + R_{3i} + dR_3)(R_1 + R_4)} \cong \frac{R_2 R_{3i}}{(R_2 + R_{3i})^2} \left(\frac{dR_3}{R_{3i}} \right)$$


Since $\frac{dR_3 / R_3}{\epsilon_a} = GF$ and $R_2 = R_{3i}$, therefore $\frac{V_o}{V_s} = \frac{1}{4} \epsilon_a GF$

Or the sensitivity

$$\frac{V_o}{\epsilon_a} = \frac{1}{4} V_s GF$$

(in unit of V/ppm)

Installation of One Active Gage

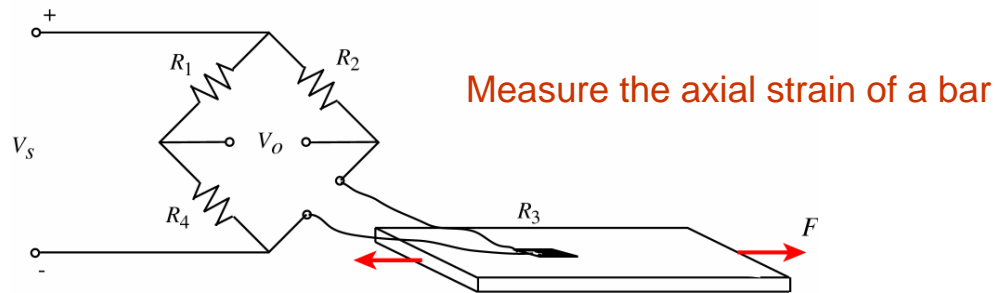


Ex: If under tension the output voltage is $V_o = 2.1 \text{ mV}$. Given $V_s = 10 \text{ V}$ and $GF = 1.8$, determine the measured strain ϵ_a .

From the sensitivity, we obtain

$$\epsilon_a = \frac{4V_o}{V_s GF} = \frac{4 \times 2.1 \times 10^{-3}}{10 \times 1.8} = 0.000933, \text{ or } 933 \text{ ppm}$$

Half Bridge Circuit (two active gages)

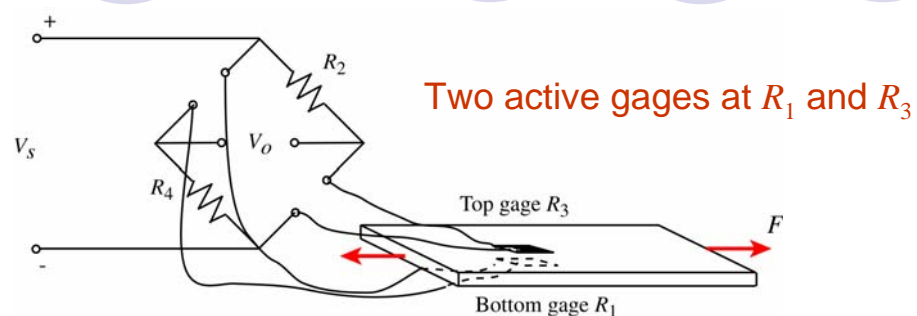

Initially balance the gage, hence $R_{3i}R_{1i} = R_4R_2$.

When loaded, we can get the output voltage per input voltage as

$$\frac{V_o}{V_s} \approx \frac{R_2 R_{3i}}{(R_2 + R_{3i})^2} \left(\frac{dR_1}{R_{1i}} + \frac{dR_3}{R_{3i}} \right) \quad \text{where} \quad \frac{dR_1}{R_{1i}} = \frac{dR_3}{R_{3i}} = \epsilon_a GF$$


Therefore the sensitivity for this case is

$$\boxed{\frac{V_o}{\epsilon_a} = \frac{2}{4} V_s GF}$$

Change of R in Bridge Circuit



If all four resistors R in bridge circuit have a change,
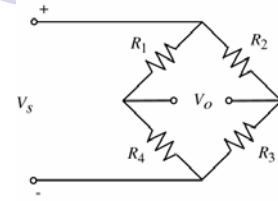
$$\frac{V_o}{V_s} \approx \frac{R_2 R_{3i}}{(R_2 + R_{3i})^2} \left(\frac{dR_1}{R_{1i}} - \frac{dR_2}{R_{2i}} + \frac{dR_3}{R_{3i}} - \frac{dR_4}{R_{4i}} \right)$$



- As strain increased, dR_1 and dR_3 contribute to $+V_o$ whereas dR_2 and dR_4 contribute to $-V_o$.
- According to the \pm signs, it is important where you place strain gages in the circuit.
- For the previous ex., if we put the first gage at R_1 , it does not make sense to put the second gage at R_2 and R_4 , because dR could cancel and V_o is zero.

Strain In a Transverse Beam

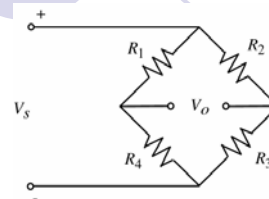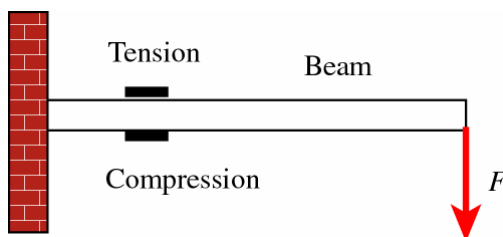


$$\frac{V_o}{V_s} \approx \frac{R_2 R_{3i}}{(R_2 + R_{3i})^2} \left(\frac{dR_1}{R_{1i}} - \frac{dR_2}{R_{2i}} + \frac{dR_3}{R_{3i}} - \frac{dR_4}{R_{4i}} \right)$$

For a little exercise, if we have two active gages on a beam as shown, where to connect these two gages in the Wheatstone bridge?

Note that the resistance change due to compression is minus of that in tension.

Answer: At 1 and 2, 3 and 4, 2 and 3, or 1 and 4, else result in zero output voltage.

Temperature Compensation

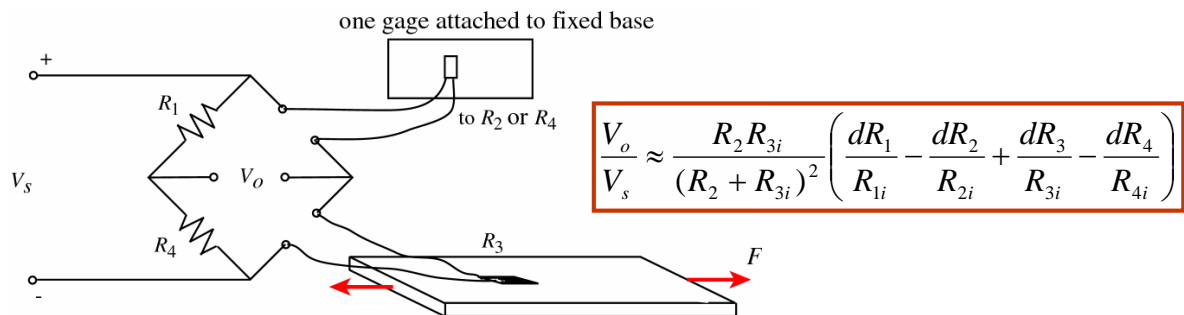


To cancel the resistance change of the strain gages due to thermal effect, we can setup the gages as shown.

With R_3 as an active gage, we can use R_2 or R_4 to compensate for the temperature.

Full Bridge Circuit (four active gages)
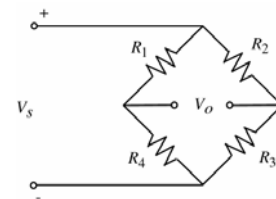
$$\frac{V_o}{V_s} \approx \frac{R_2 R_{3i}}{(R_2 + R_{3i})^2} \left(\frac{dR_1}{R_{1i}} - \frac{dR_2}{R_{2i}} + \frac{dR_3}{R_{3i}} - \frac{dR_4}{R_{4i}} \right)$$



When all R on the bridge are replaced by strain gages:

" R_1 and R_3 must have positive strain (tension), while R_2 and R_4 have negative strain (compression)".

We can get the sensitivity four times of the quarter bridge and two times of the half bridge.

Bridge Constant (K)

Defined as output of the bridge per output of the primary (one active) gage.

For one active gage ($K=1$),
the sensitivity is

$$\frac{V_0}{\varepsilon_a} = \frac{1}{4} V_s GF$$

For two active gages ($K=2$),
the sensitivity is

$$\frac{V_0}{\varepsilon_a} = \frac{2}{4} V_s GF$$

For four active gages ($K=4$),
the sensitivity is

$$\frac{V_0}{\varepsilon_a} = \frac{4}{4} V_s GF$$

$$\frac{V_0}{\varepsilon_a} = \frac{K}{4} V_s GF$$