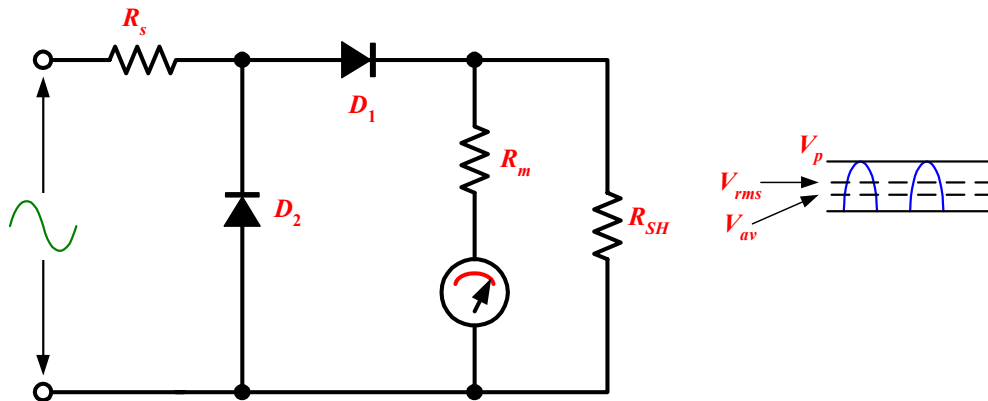


AC Voltmeter: PMMC Based

Example: A PMMC instrument has FSD of $100\ \mu\text{A}$ and a coil resistance of $1700\ \Omega$ is used in the half-wave rectifier voltmeter. The silicon diode (D_1) must have a minimum (peak) forward current of $100\ \mu\text{A}$. When the measured voltage is 20% of FSD. The voltmeter is to indicate $50\ \text{V}_{\text{rms}}$ at full scale Calculate the values of R_S and R_{SH} .


Known: FSD of I_m R_m

Solution: $R_S = 139.5\ \text{k}\Omega$ $R_{SH} = 778\ \Omega$



AC Voltmeter: PMMC Based

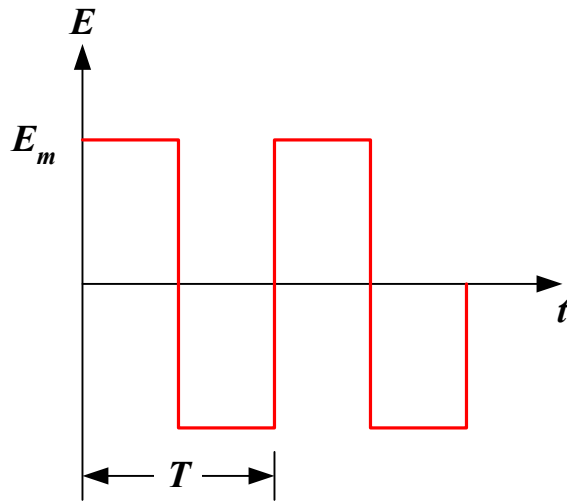
Example The symmetrical square-wave voltage is applied to an average-responding ac voltmeter with a scale calibrated in terms of the rms value of a sine wave. If the voltmeter is the full-wave rectified configuration. Calculate the error in the meter indication. Neglect all voltage drop in all diodes.



Solution 11%


Bridge Circuit

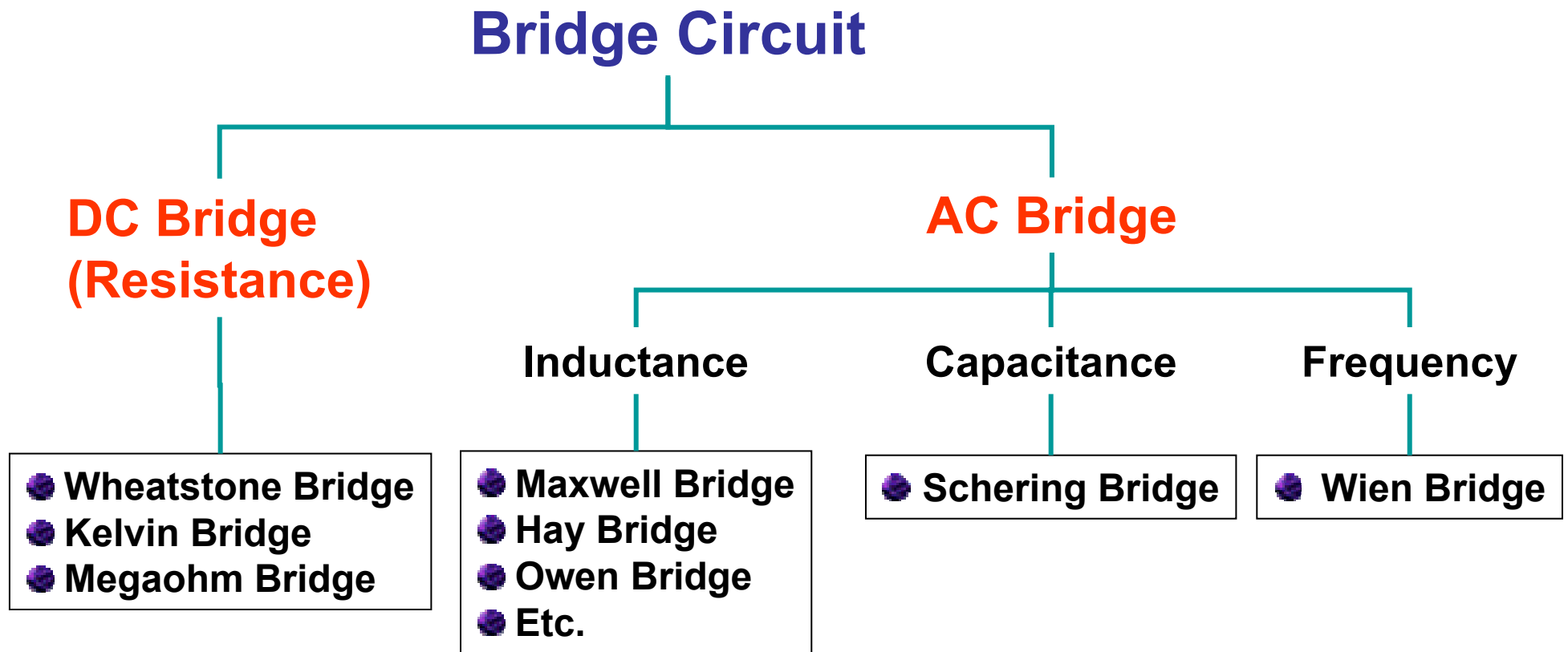Bridge Circuit is a null method, operates on the principle of comparison. That is a known (standard) value is adjusted until it is equal to the unknown value.



Wheatstone Bridge and Balance Condition

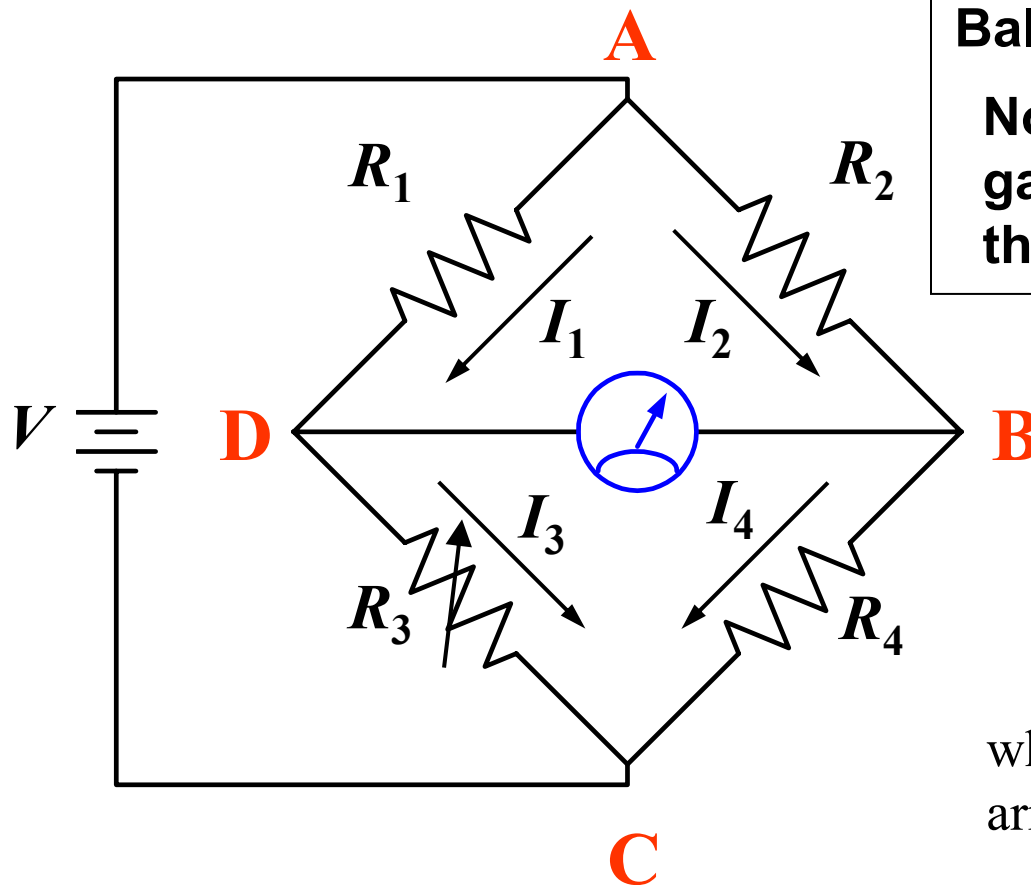The standard resistor R_3 can be adjusted to null or balance the circuit.



Balance condition:

No potential difference across the galvanometer (there is no current through the galvanometer)

Under this condition: $V_{AD} = V_{AB}$

$$I_1 R_1 = I_2 R_2$$


And also $V_{DC} = V_{BC}$

$$I_3 R_3 = I_4 R_4$$


where I_1 , I_2 , I_3 , and I_4 are current in resistance arms respectively, since $I_1 = I_3$ and $I_2 = I_4$

$$\frac{R_1}{R_3} = \frac{R_2}{R_4} \quad \text{or} \quad R_x = R_4 = R_3 \frac{R_2}{R_1}$$


Example

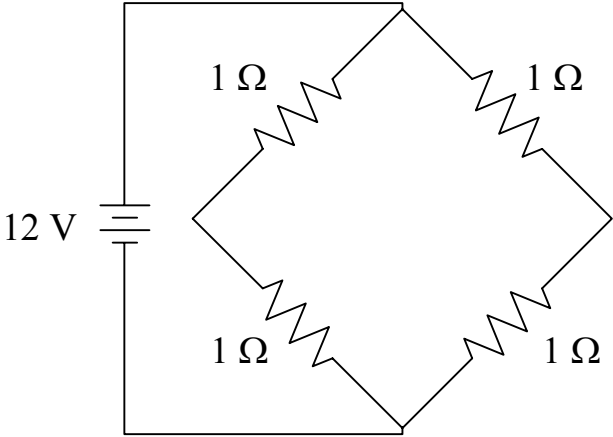


(a) Equal resistance

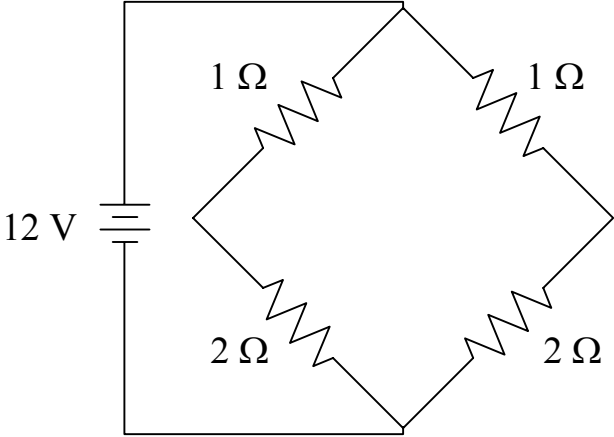

(b) Proportional resistance

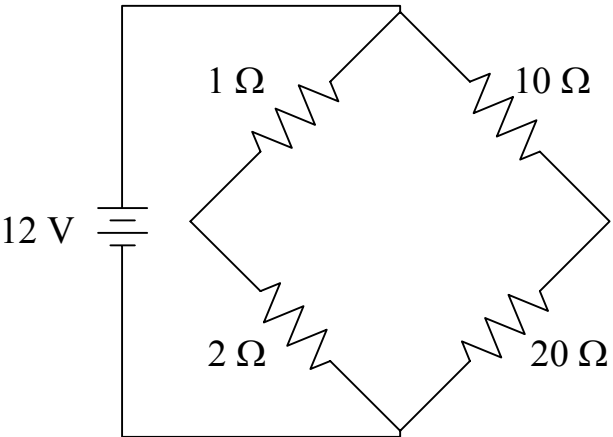

(c) Proportional resistance

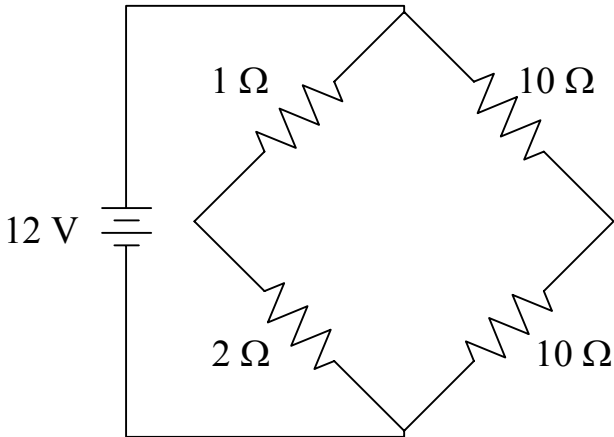


(d) 2-Volt unbalance

Sensitivity of Galvanometer

A galvanometer is used to detect an unbalance condition in Wheatstone bridge. Its sensitivity is governed by: **Current sensitivity (currents per unit deflection) and internal resistance.**

consider a bridge circuit under a small unbalance condition, and apply circuit analysis to solve the current through galvanometer

Thévenin Equivalent Circuit

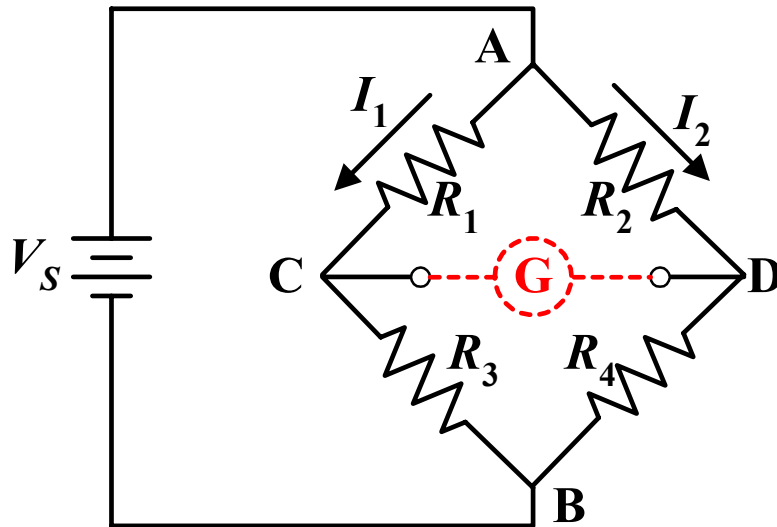

Thévenin Voltage (V_{TH})

$$V_{CD} = V_{AC} - V_{AD} = I_1 R_1 - I_2 R_2$$


$$\text{where } I_1 = \frac{V}{R_1 + R_3} \text{ and } I_2 = \frac{V}{R_2 + R_4}$$

Therefore

$$V_{TH} = V_{CD} = V \left(\frac{R_1}{R_1 + R_3} - \frac{R_2}{R_2 + R_4} \right)$$


Sensitivity of Galvanometer (continued)

Thévenin Resistance (R_{TH})

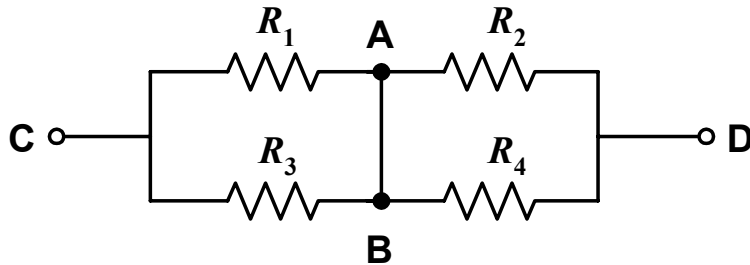

$$R_{TH} = R_1 // R_3 + R_2 // R_4$$

Completed Circuit

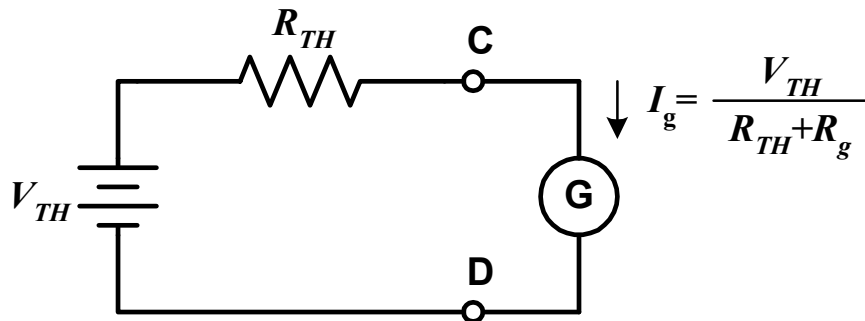


$$I_g = \frac{V_{TH}}{R_{TH} + R_g}$$


where I_g = the galvanometer current
 R_g = the galvanometer resistance

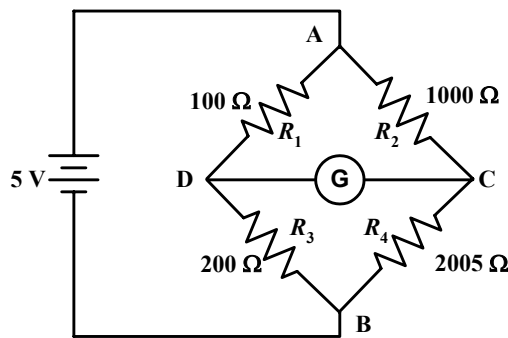Example 1 Figure below show the schematic diagram of a Wheatstone bridge with values of the bridge elements. The battery voltage is 5 V and its internal resistance negligible. The galvanometer has a current sensitivity of 10 mm/ μ A and an internal resistance of 100 Ω . Calculate the deflection of the galvanometer caused by the 5- Ω unbalance in arm BC


SOLUTION The bridge circuit is in the small unbalance condition since the value of resistance in arm BC is 2,005 Ω .



(a)

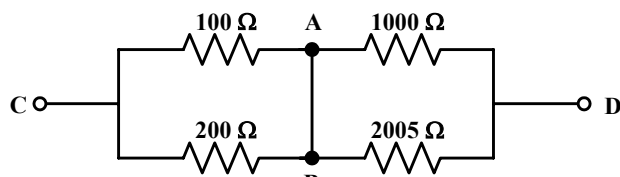

(b)

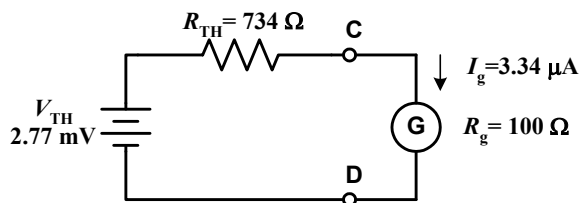

(c)

Thévenin Voltage (V_{TH})

$$V_{TH} = V_{AD} - V_{AC} = 5 \text{ V} \times \left(\frac{100}{100 + 200} - \frac{1000}{1000 + 2005} \right) \approx 2.77 \text{ mV}$$

Thévenin Resistance (R_{TH})

$$R_{TH} = 100 // 200 + 1000 // 2005 = 734 \Omega$$

The galvanometer current

$$I_g = \frac{V_{TH}}{R_{TH} + R_g} = \frac{2.77 \text{ mV}}{734 \Omega + 100 \Omega} = 3.32 \mu\text{A}$$

Galvanometer deflection


$$d = 3.32 \mu\text{A} \times \frac{10 \text{ mm}}{\mu\text{A}} = 33.2 \text{ mm}$$

Example 2 The galvanometer in the previous example is replaced by one with an internal resistance of $500\ \Omega$ and a current sensitivity of $1\text{mm}/\mu\text{A}$. Assuming that a deflection of $1\ \text{mm}$ can be observed on the galvanometer scale, determine if this new galvanometer is capable of detecting the $5\text{-}\Omega$ unbalance in arm BC

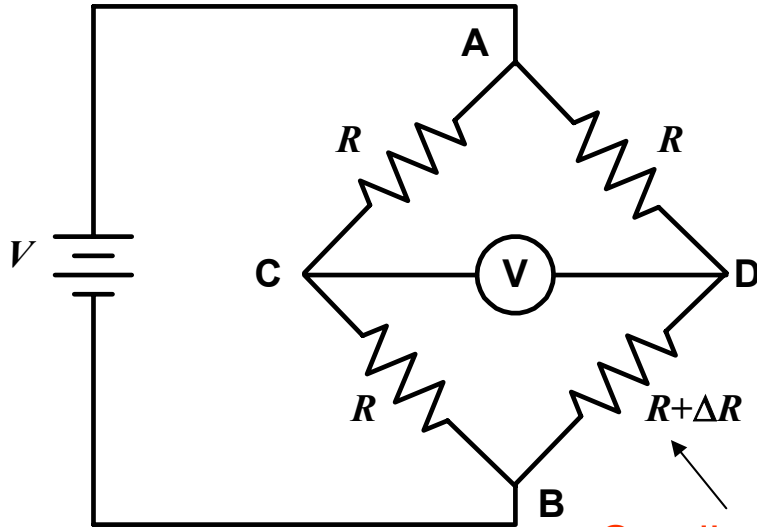Example 3 If all resistances in the Example 1 increase by 10 times, and we use the galvanometer in the Example 2. Assuming that a deflection of $1\ \text{mm}$ can be observed on the galvanometer scale, determine if this new setting can be detected (the $50\text{-}\Omega$ unbalance in arm BC)

Deflection Method

Consider a bridge circuit which have identical resistors, R in three arms, and the last arm has the resistance of $R + \Delta R$. if $\Delta R/R \gg 1$



Small unbalance occur by the external environment

Thévenin Voltage (V_{TH})

$$V_{TH} = V_{CD} = V \frac{\Delta R / R}{4 + 2\Delta R / R}$$


Thévenin Resistance (R_{TH})

$$R_{TH} \approx R$$


In an unbalanced condition, the magnitude of the current or voltage drop for the meter or galvanometer portion of a bridge circuit is a direct indication of the change in resistance in one arm.

This kind of bridge circuit can be found in sensor applications, where the resistance in one arm is sensitive to a physical quantity such as pressure, temperature, strain etc.

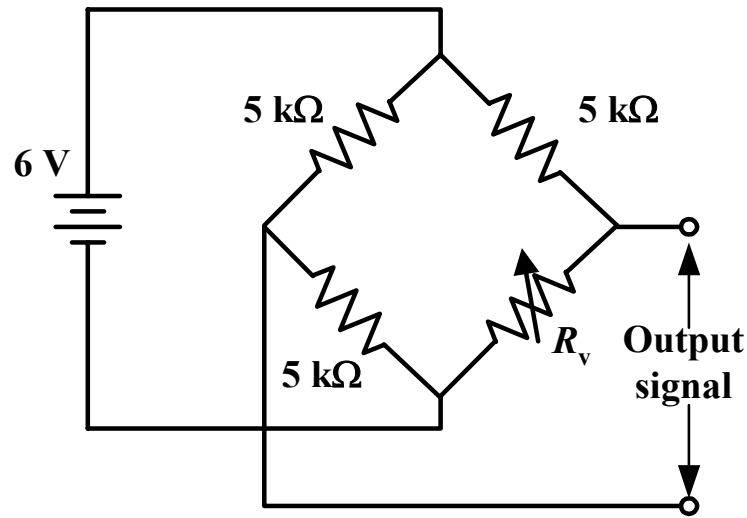Example Circuit in Figure (a) below consists of a resistor R_v which is sensitive to the temperature change. The plot of R VS $Temp.$ is also shown in Figure (b). Find (a) the temperature at which the bridge is balance and (b) The output signal at Temperature of 60°C .




(a)

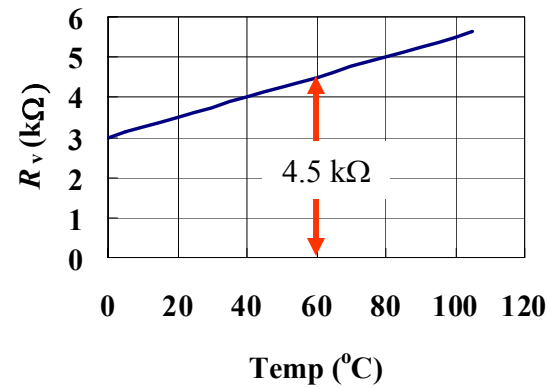

(b)

AC Bridge: Balance Condition

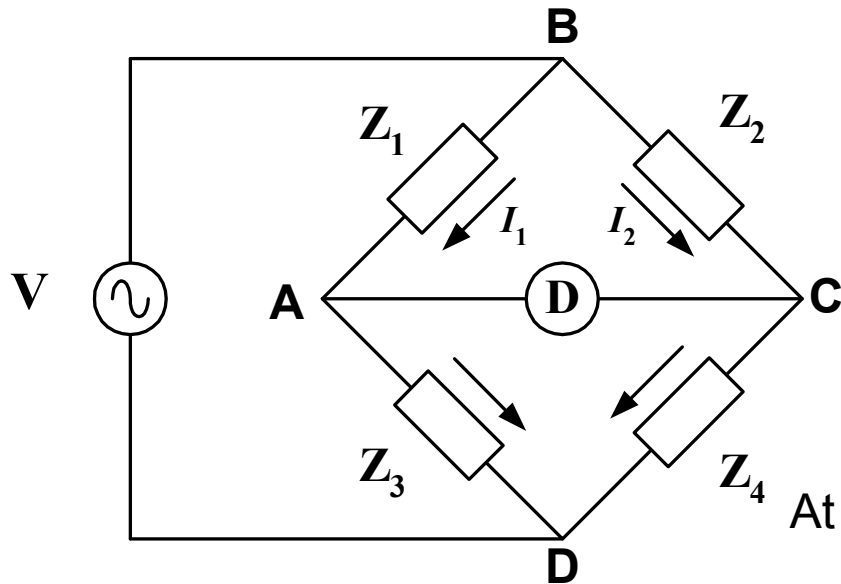

- all four arms are considered as impedance (frequency dependent components)
- The detector is an ac responding device: headhone, ac meter
- Source: an ac voltage at desired frequency

Z_1, Z_2, Z_3 and Z_4 are the impedance of bridge arms

At balance point: $E_{BA} = E_{BC}$ or $I_1 Z_1 = I_2 Z_2$

$$I_1 = \frac{V}{Z_1 + Z_3} \text{ and } I_2 = \frac{V}{Z_2 + Z_4}$$

General Form of the ac Bridge

Complex Form:

$$Z_1 Z_4 = Z_2 Z_3$$

Polar Form:

$$Z_1 Z_4 (\angle \theta_1 + \angle \theta_4) = Z_2 Z_3 (\angle \theta_2 + \angle \theta_3)$$

Magnitude balance:

$$Z_1 Z_4 = Z_2 Z_3$$

Phase balance:

$$\angle \theta_1 + \angle \theta_4 = \angle \theta_2 + \angle \theta_3$$

Example The impedance of the basic ac bridge are given as follows:

$$\mathbf{Z}_1 = 100 \, \Omega \angle 80^\circ \text{ (inductive impedance)}$$


$$\mathbf{Z}_2 = 250 \, \Omega \text{ (pure resistance)}$$

$$\mathbf{Z}_3 = 400 \angle 30^\circ \Omega \text{ (inductive impedance)}$$

$$\mathbf{Z}_4 = \text{unknown}$$

Determine the constants of the unknown arm.

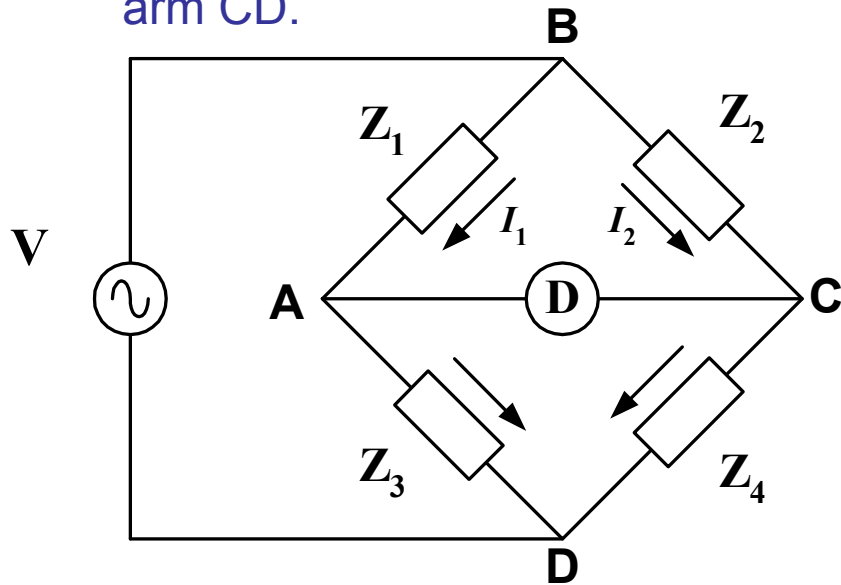Example an ac bridge is in balance with the following constants: arm AB, $R = 200 \Omega$ in series with $L = 15.9 \text{ mH}$; arm BC, $R = 300 \Omega$ in series with $C = 0.265 \mu\text{F}$; arm CD, unknown; arm DA, $= 450 \Omega$. The oscillator frequency is 1 kHz. Find the constants of arm CD.



SOLUTION

$$Z_1 = R + j\omega L = 200 + j100 \Omega$$


$$Z_2 = R + 1/j\omega C = 300 - j600 \Omega$$

$$Z_3 = R = 450 \Omega$$


$$Z_4 = \text{unknown}$$

The general equation for bridge balance states that $Z_1 Z_4 = Z_2 Z_3$

Operational Amplifier: Op Amp

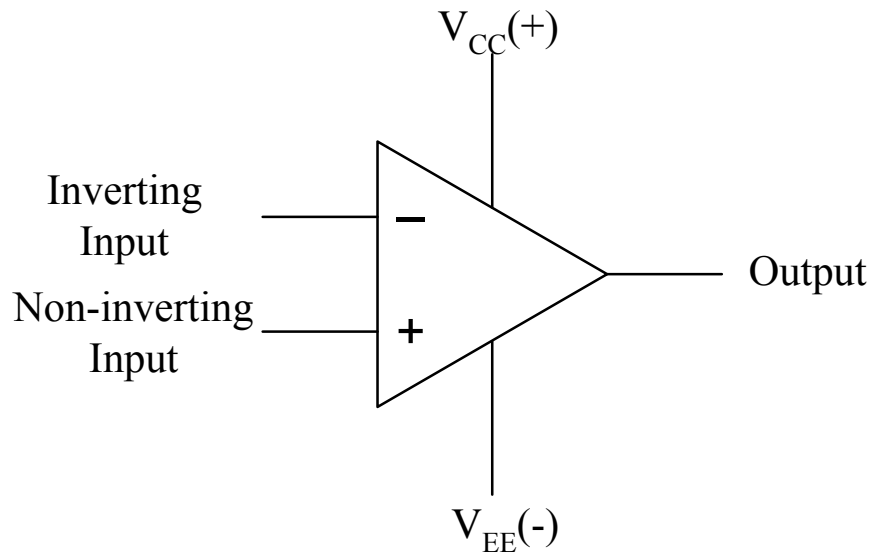

(a) Electrical Symbol for the op amp

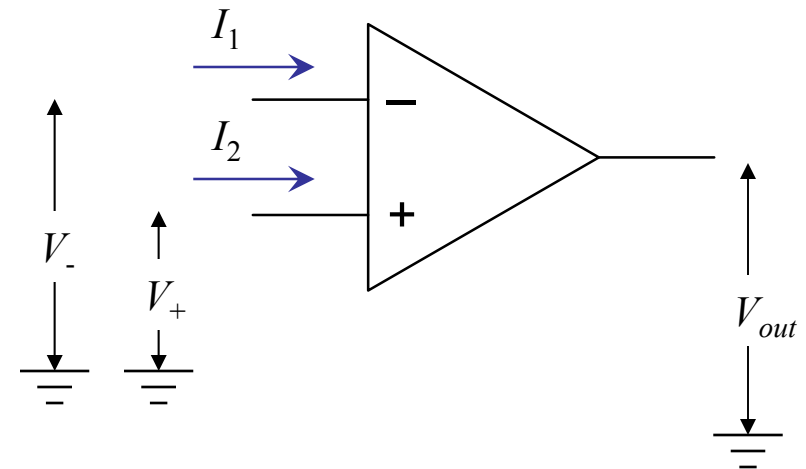

(b) Minimum connections to an op amp


Ideal Op Amp Rules:

1. No current flows in to either input terminal
2. There is no voltage difference between the two input terminals

Rule 1: $I_1 = I_2 = 0$; $R_{+/-} = \infty$

Rule 2: $V_+ = V_-$; **Virtually shorted**

Inverting Amplifier

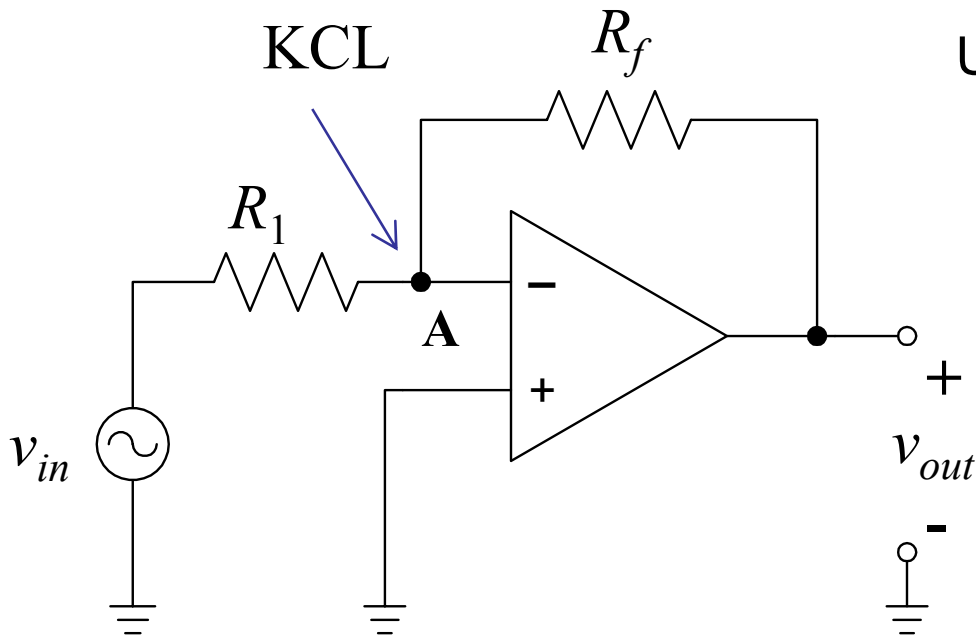

Use KCL at point A and apply Rule 1:
(no current flows into the inverting input)

$$\frac{v_A - v_{in}}{R_1} + \frac{v_A - v_{out}}{R_f} = 0$$

Rearrange


$$v_A \left(\frac{1}{R_1} + \frac{1}{R_f} \right) - \left(\frac{v_{in}}{R_1} + \frac{v_{out}}{R_f} \right) = 0$$

Apply Rule 2: (no voltage difference between inverting and non-inverting inputs)

Since V_+ at zero volts, therefore V_- is also at zero volts too.

$$v_A = 0$$

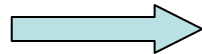
$$\frac{v_{in}}{R_1} + \frac{v_{out}}{R_f} = 0$$



$$\frac{v_{out}}{v_{in}} = -\frac{R_f}{R_1}$$

Inverting Amplifier: another approach

No current flows into op amp

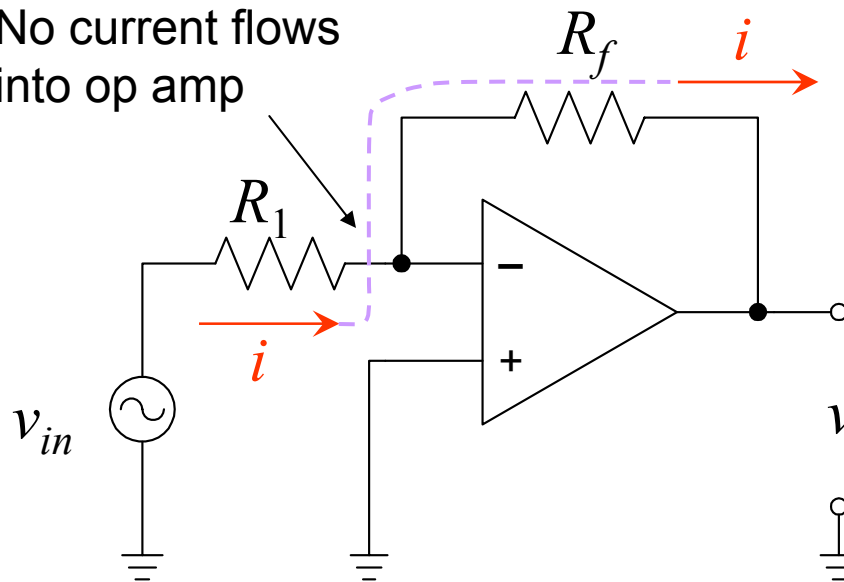

From Rule 2: we know that $V^- = V^+ = 0$, and therefore

$$-v_{in} + iR_1 - \cancel{0} = 0 \quad \Rightarrow \quad i = \frac{v_{in}}{R_1}$$

Since there is no current into op amp (Rule 1)


$$-\cancel{0} + iR_f + v_{out} = 0 \quad \Rightarrow \quad v_{out} = -iR_f$$

Combine the results, we get


$$\frac{v_{out}}{v_{in}} = -\frac{R_f}{R_1}$$

Given $v_{in} = 5\sin 3t$, $R_1 = 4.7 \text{ k}\Omega$ and $R_f = 47 \text{ k}\Omega$
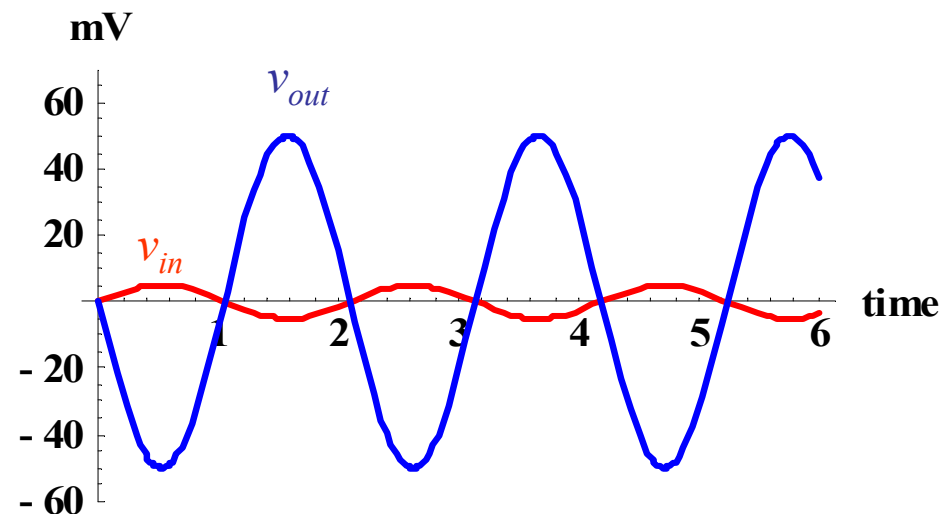
$$v_{out} = -10v_{in} = -50 \sin 3t \quad \text{mV}$$



Non-inverting Amplifier

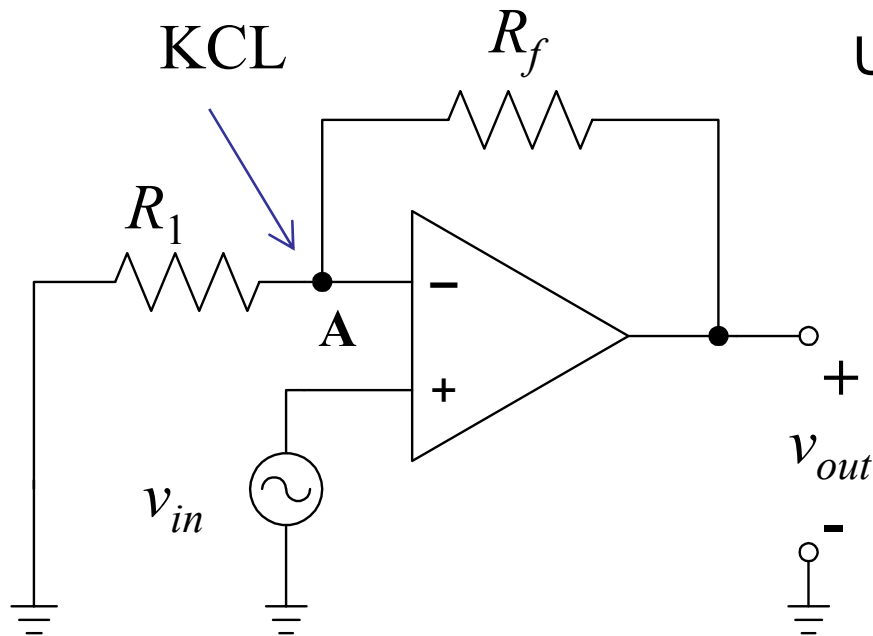

Use KCL at point A and apply Rule 1:


$$\frac{v_A}{R_1} + \frac{v_A - v_{out}}{R_f} = 0$$

Apply Rule 2: $v_{in} = v_A$

$$\frac{v_{out}}{v_{in}} = 1 + \frac{R_f}{R_1}$$


Given $v_{in} = 5\sin 3t$, $R_1 = 4.7 \text{ k}\Omega$ and $R_f = 47 \text{ k}\Omega$
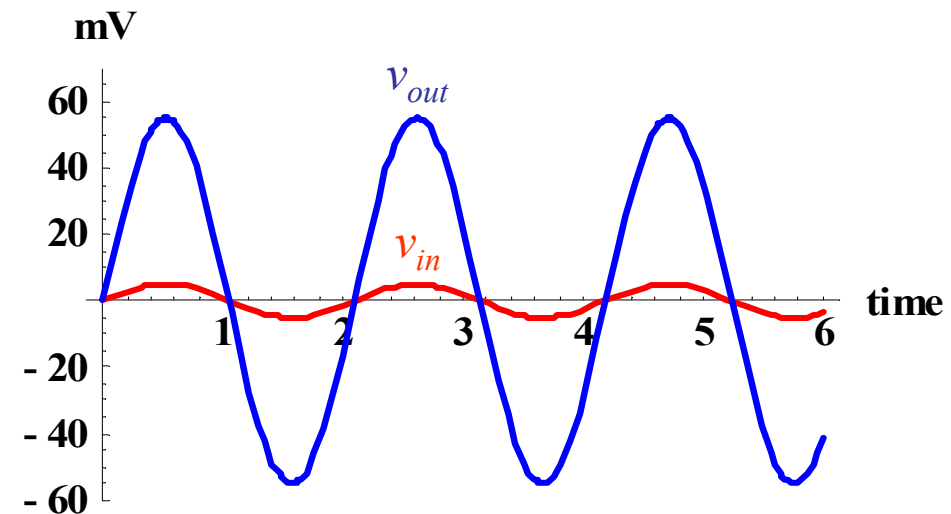
$$v_{out} = 11v_{in} = 55 \sin 3t \quad \text{mV}$$



Summing Amplifier: Mathematic Operation

$$i = i_1 + i_2 + i_3$$

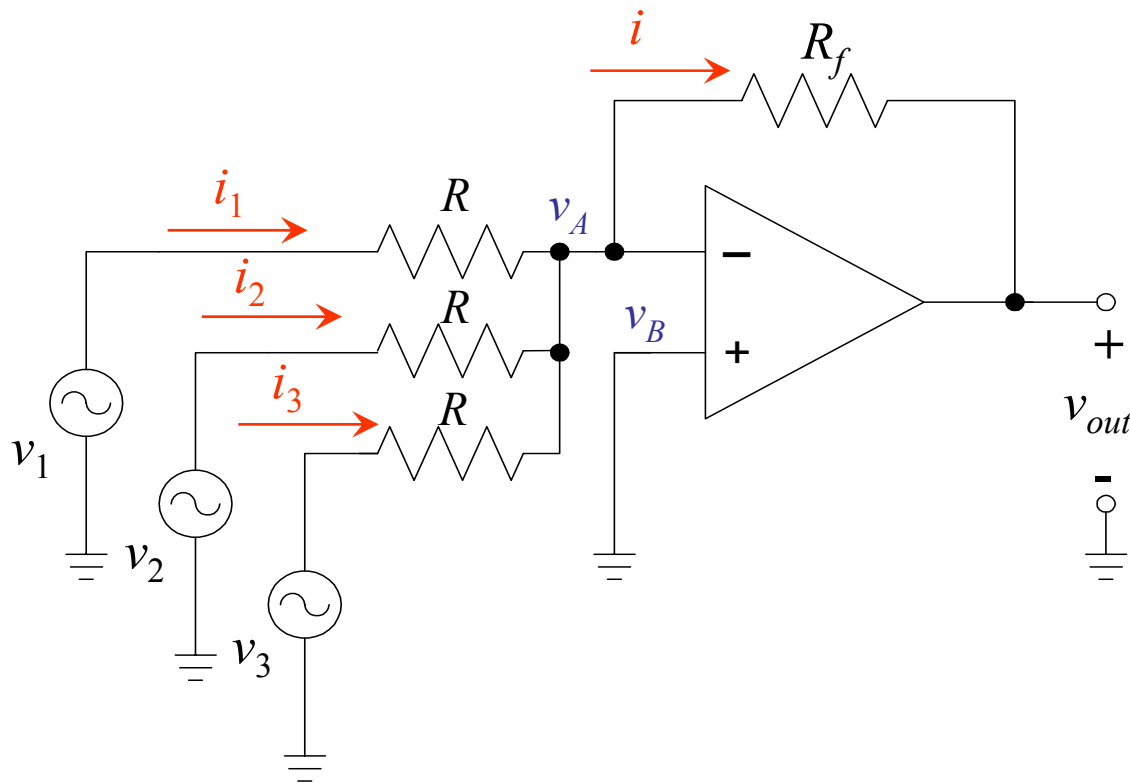

Use KCL and apply Rule 1:


$$\frac{v_A - v_1}{R} + \frac{v_A - v_2}{R} + \frac{v_A - v_3}{R} + \frac{v_A - v_{out}}{R_f} = 0$$

Since $v_A = 0$ (Rule 2)

$$v_{out} = -\frac{R_f}{R}(v_1 + v_2 + v_3)$$

Sum of v_1 , v_2 and v_3

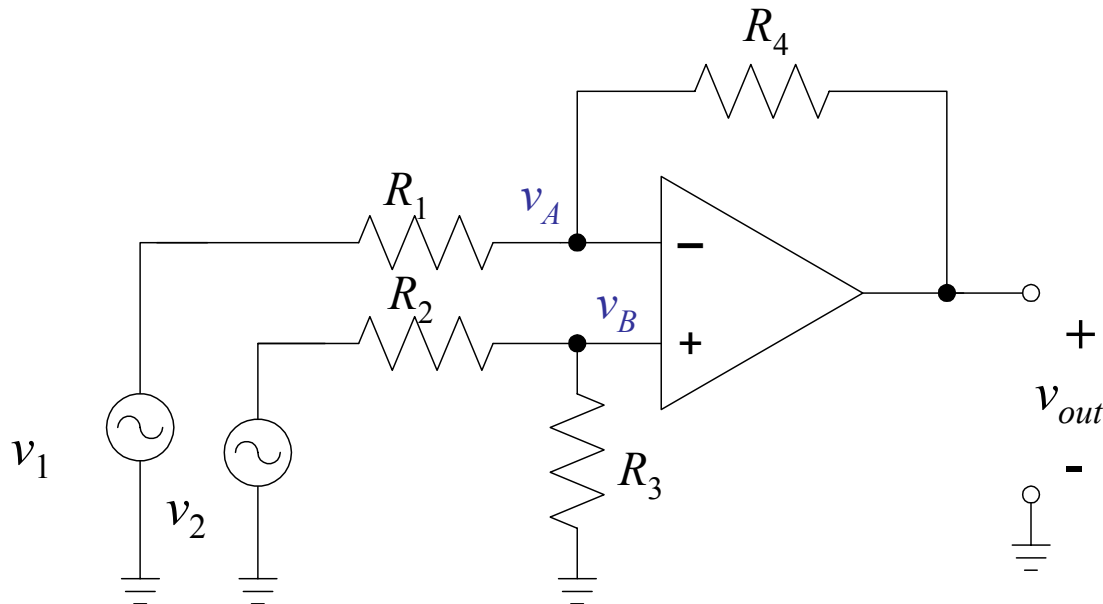Difference Amplifier: Mathematic Operation



Use KCL and apply Rule 1:

$$\frac{v_A - v_1}{R_1} + \frac{v_A - v_{out}}{R_4} = 0 \quad (1)$$

Since $v_A = v_B$ (Rule 2) and

$$v_A = v_B = \left(\frac{R_3}{R_2 + R_3} \right) v_2 \quad (2)$$

Substitute eq. (2) into eq. (1), we get


$$\frac{v_{out}}{R_4} = \left(\frac{R_1 + R_4}{R_1 R_4} \right) \left(\frac{R_3}{R_2 + R_3} \right) v_2 - \frac{v_1}{R_1}$$

If $R_1 = R_2 = R$ and $R_3 = R_4 = R_f$

$$v_{out} = \frac{R_f}{R} (v_2 - v_1)$$

Difference of v_1 and v_2

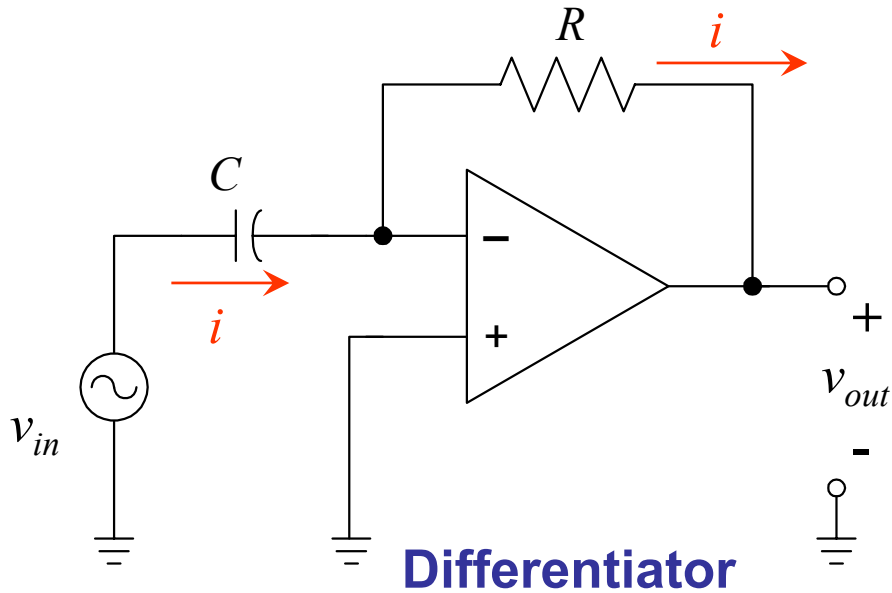
Differentiator and Integrator: Mathematic Operation



$$v_{out} = -iR$$

But $i = C \frac{dv_C}{dt}$ and $v_{in} = v_C$

$$v_{out} = -RC \frac{dv_{in}}{dt}$$

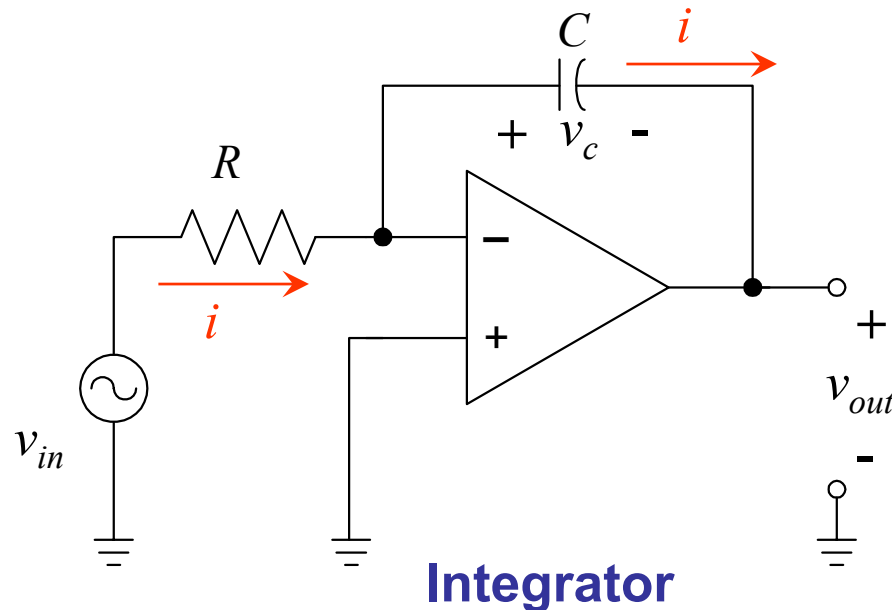

$$v_{out} = -v_C$$

But $v_C(t) = \frac{1}{C} \int_0^t i dt + v_C(0)$ and $v_{in} = iR$

$$v_{out} = -\frac{1}{RC} \int_0^t v_{in} dt + v_C(0)$$