

Digital Multimeter (DMM)



**Portable Analog
Multimeter**




Hand-held DMM



Bench-top DMM

Digital Voltmeter (DVM)

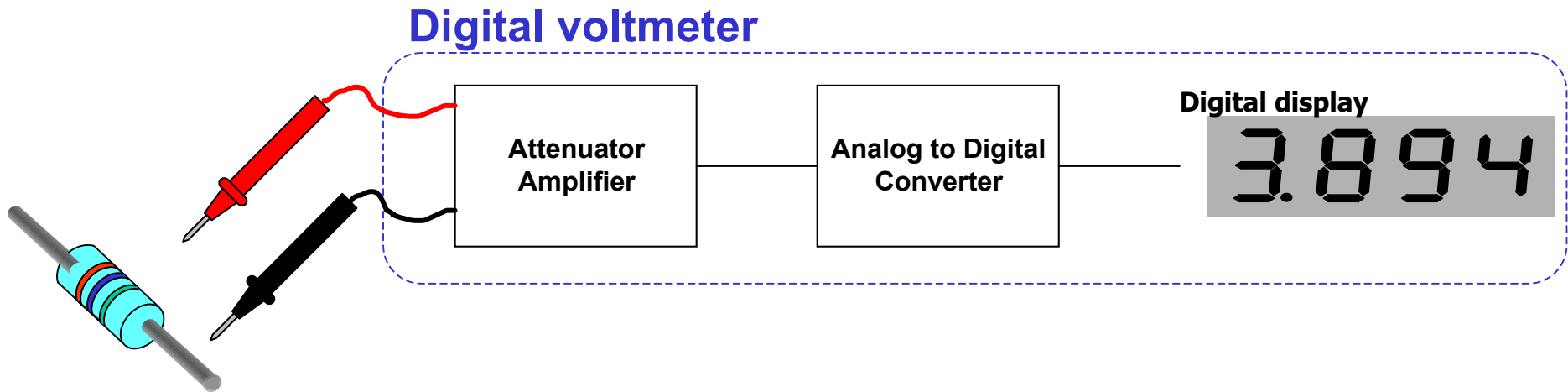
DVM is essentially an Analog to digital converter (A/D) with a digital display



**Digital MultiMeter
(DMM)**

**= electronic Volt Ohm Millimeter with
digital display**

Comparison of Digital and Analog Meter

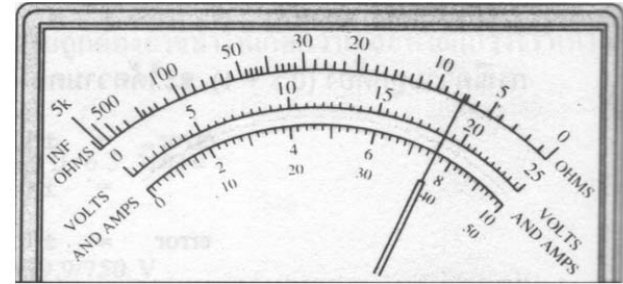

Digital meter

Leaves no doubt about the measured quantity.

Superior resolution and accuracy.

($\pm 0.5\%$ or better)

Indicates a negative quantity when the terminal polarity is reversed

No usually damaged by rough treatment

Analog meter

Wrong scale might be used or might be read incorrectly.

Inferior resolution and accuracy.

($\pm 3\%$ in common)

Pointer attempts to deflect to the left when the polarity is reversed

Can be damaged when dropped from bench level

Analog to Digital Conversion

A/D converts *an analog signal into the digital code which is proportional to the magnitude of the coming signal.*

$$V_{in} \approx k \times \text{Digital output}$$

Where k is step size or resolution

Ex. Signal from 800-1500 mV may be converted to 8-bit binary codes starting from 01010000_2 (80_{10}) to 10010110_2 (150_{10}). In this case, the step size k is equal to 10 mV.


Quantization error or Conversion error of a A/D

$$\text{Quantization error} = \frac{\text{step size}}{\text{full scale}} \times 100 = \frac{1}{2^N - 1} \times 100\%$$

Where N is the number of bit

Analog to Digital Conversion

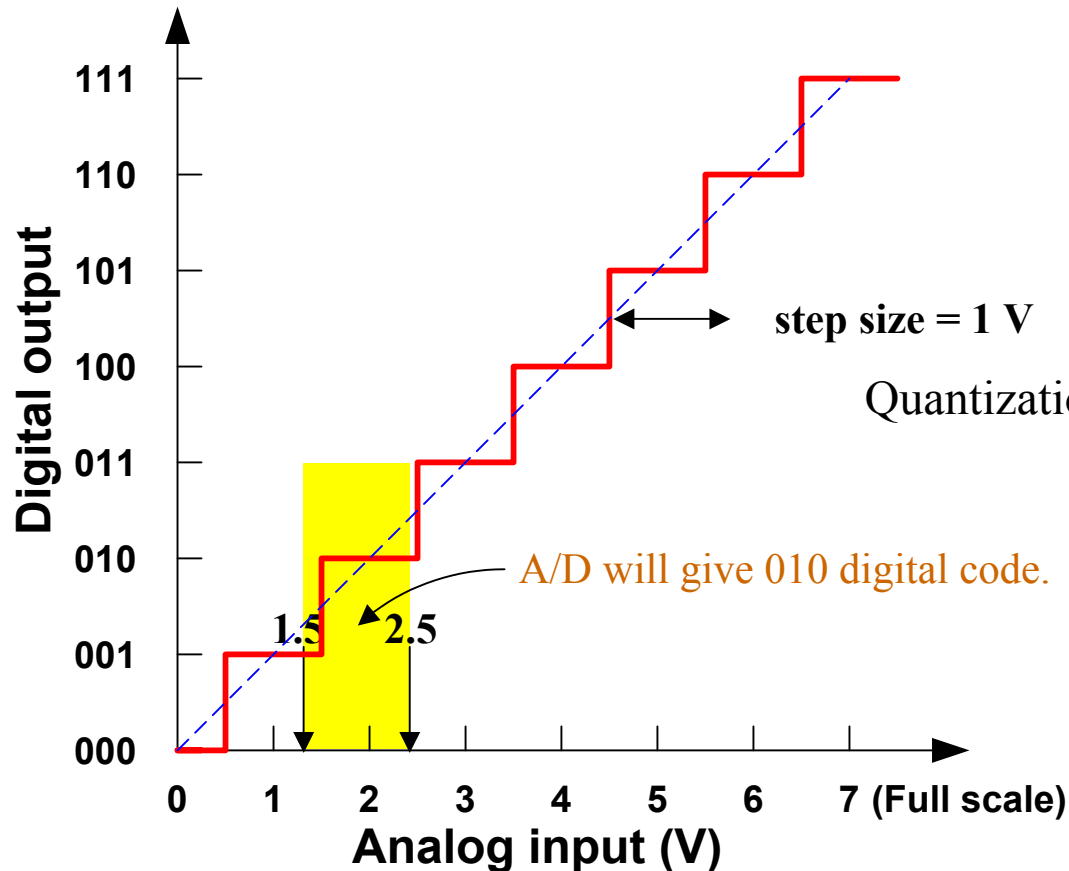Conversion time, T_c time requires to convert an analog signal to the corresponding digital code.




An example of 3 bit ADC

Ramp-type Digital Voltmeter

(also called single slope)

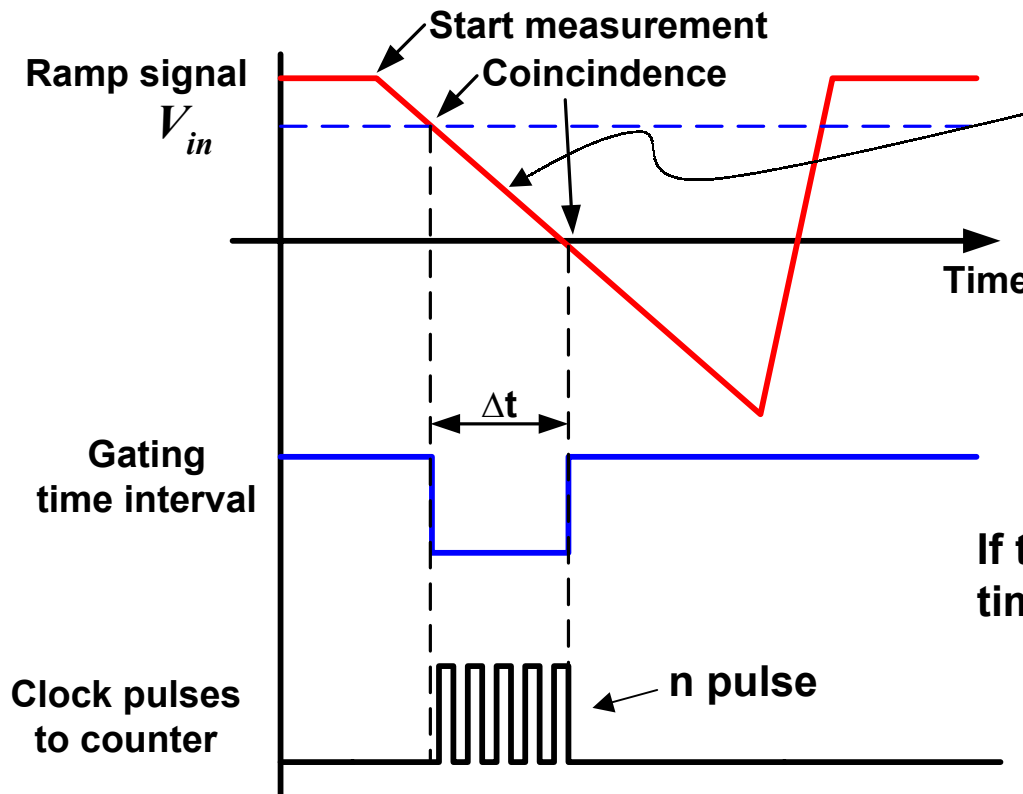Operation principle: The measurement of the time it takes for a linear ramp voltage to rise from 0 V to the level of the input voltage, or to decrease from the level of the input voltage to zero. This time interval is measured with an electronic time-interval counter.



$$V_{ramp}(t) = V_o - m t$$

Where m is the ramp rate

$$V_{ramp}(t_1) = V_{in} = V_o - m t_1$$

$$V_{ramp}(t_2) = 0 = V_o - m t_2$$

$$\Delta t = t_2 - t_1 = V_{in}/m$$

If the period of the clock is T , then during the time interval Δt , the number of pulses is

$$\Delta t \approx nT \text{ or } V_{in} \approx nmT$$



• Accuracy depends on both the ramp rate and clock period.

Voltage-to-time conversion using gated clock pulses.


Comparator

$V_+ > V_-$; $V_o = V(1)$ Logic high

$V_+ < V_-$; $V_o = V(0)$ Logic low

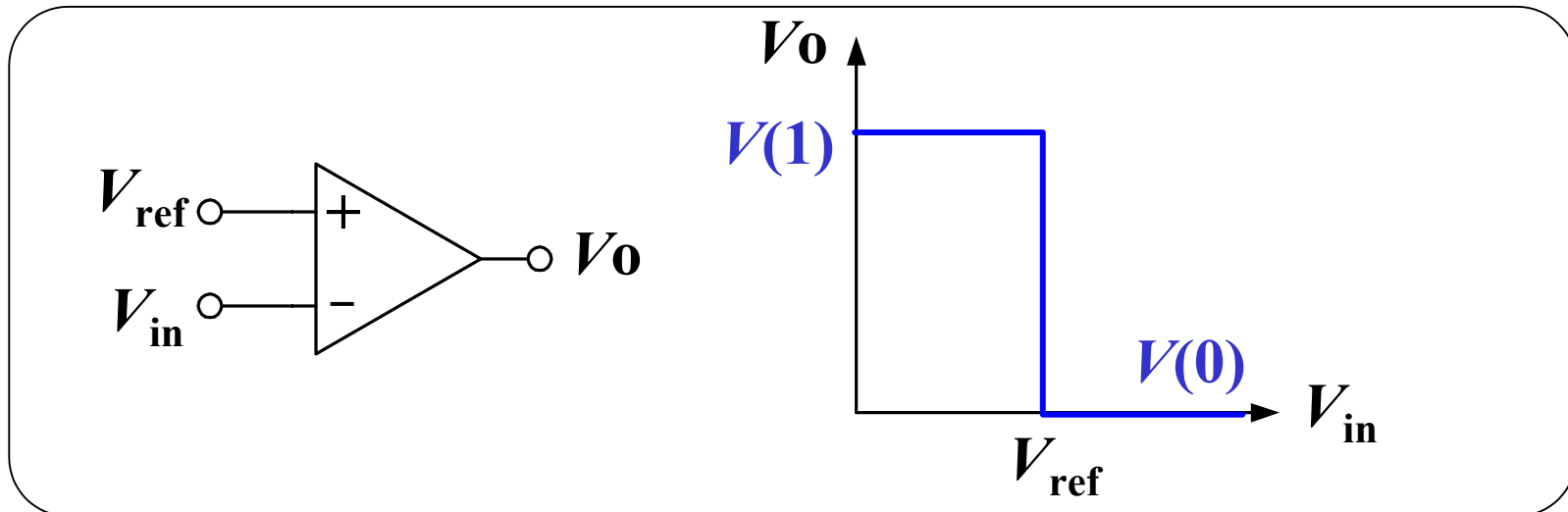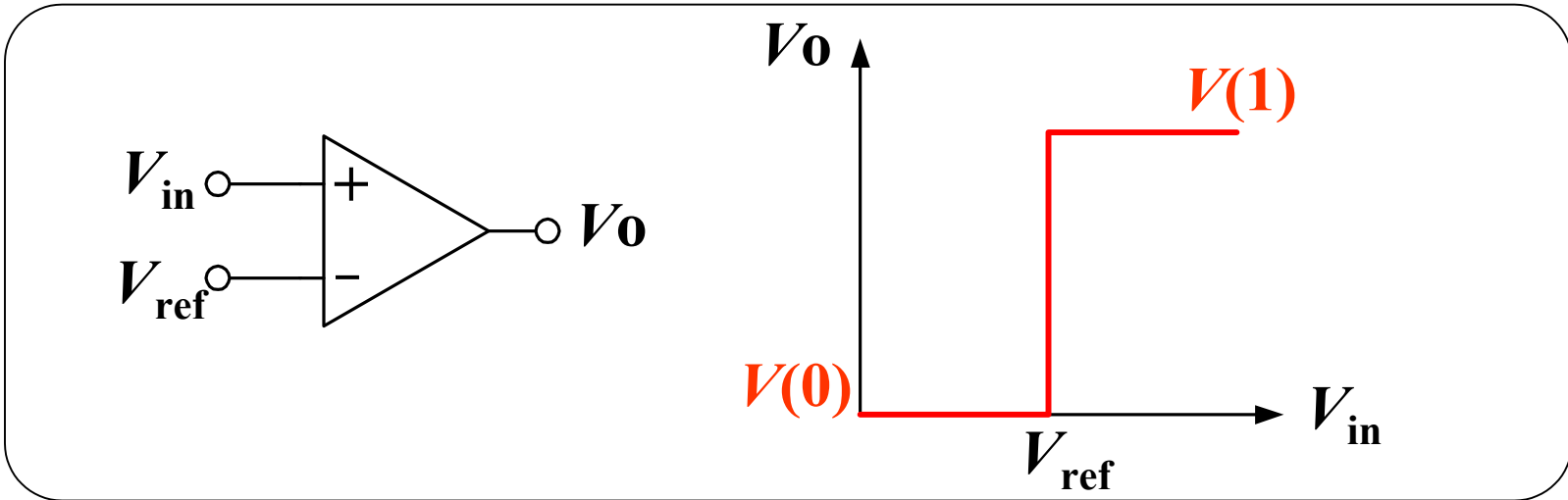

Ramp-type Digital Voltmeter

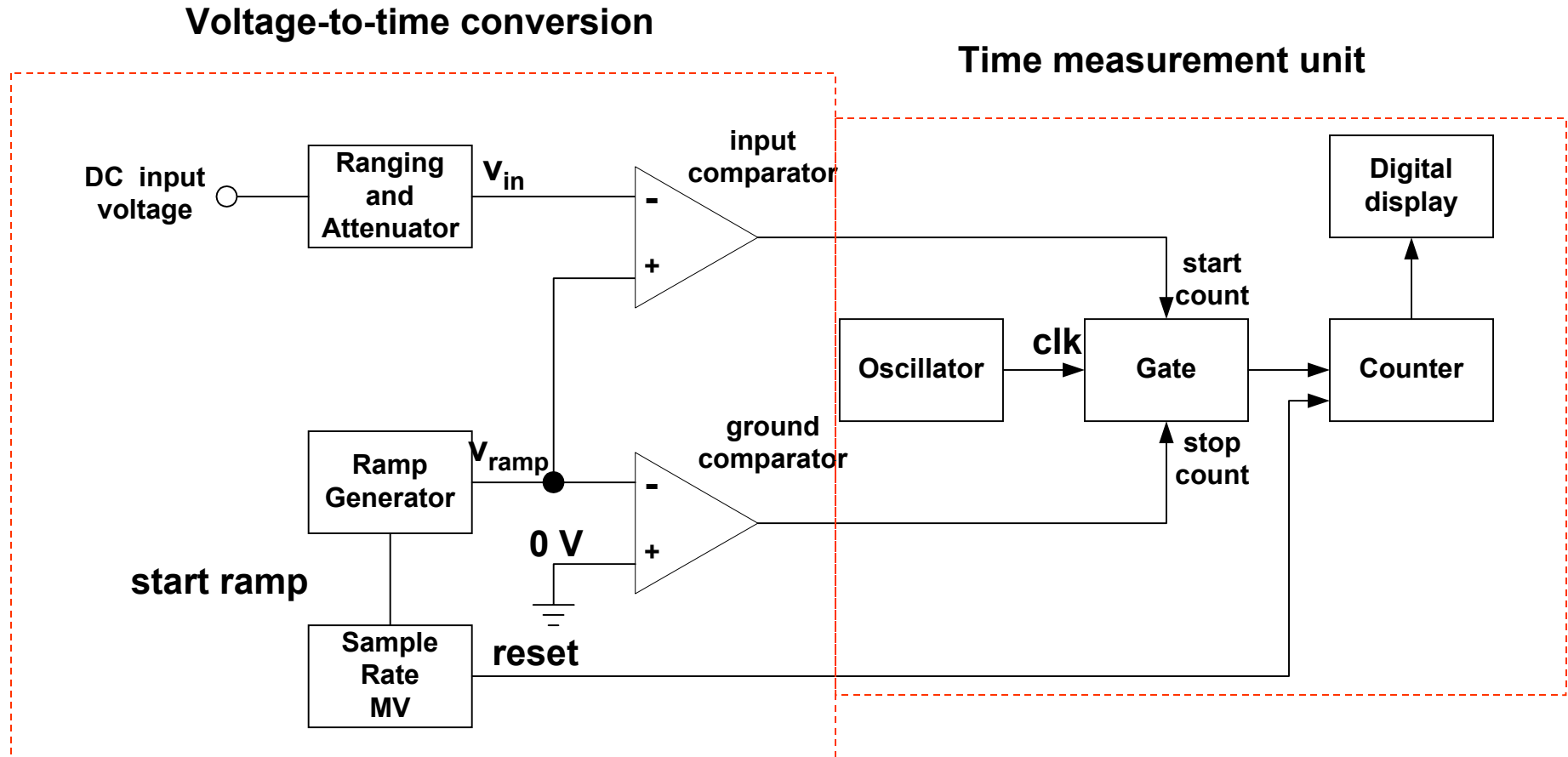


Block diagram of a ramp-type digital voltmeter.

Staircase Ramp Digital Voltmeter

(also called digital ramp)

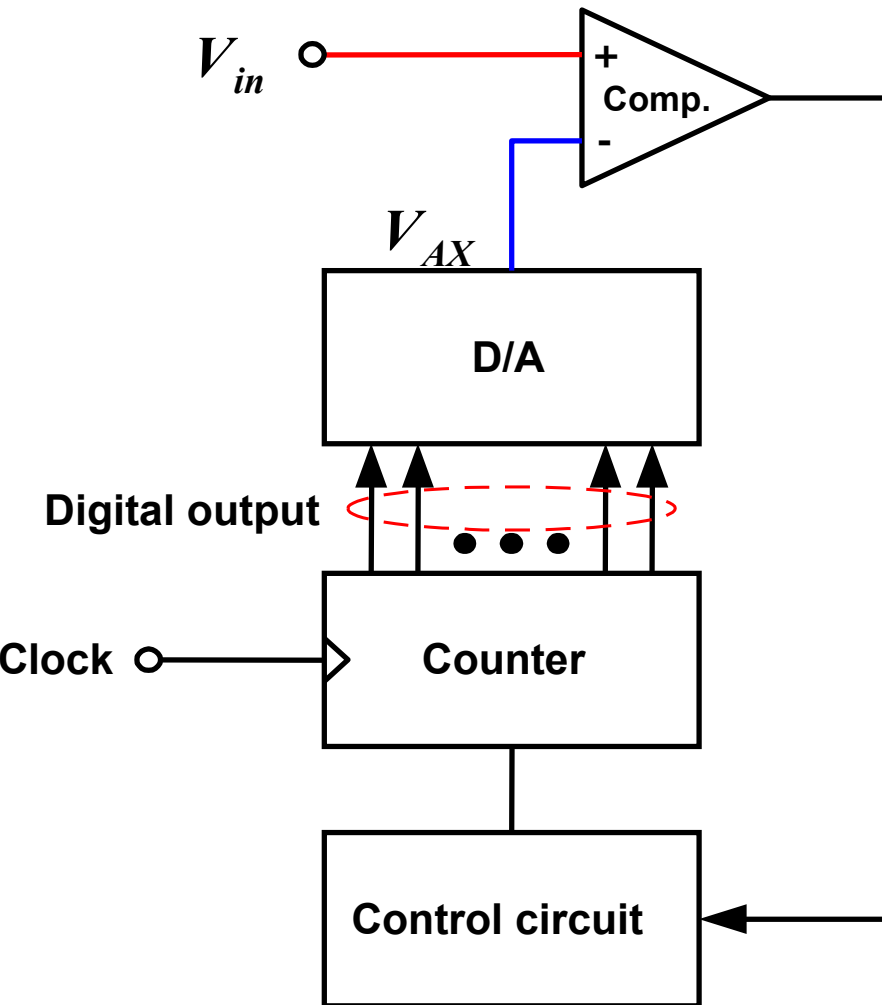
Compare the input voltage to the internally generated staircase ramp.



Block diagram

- The most simple A/D
- Slow conversion and conversion time depends on the magnitude of input signal.
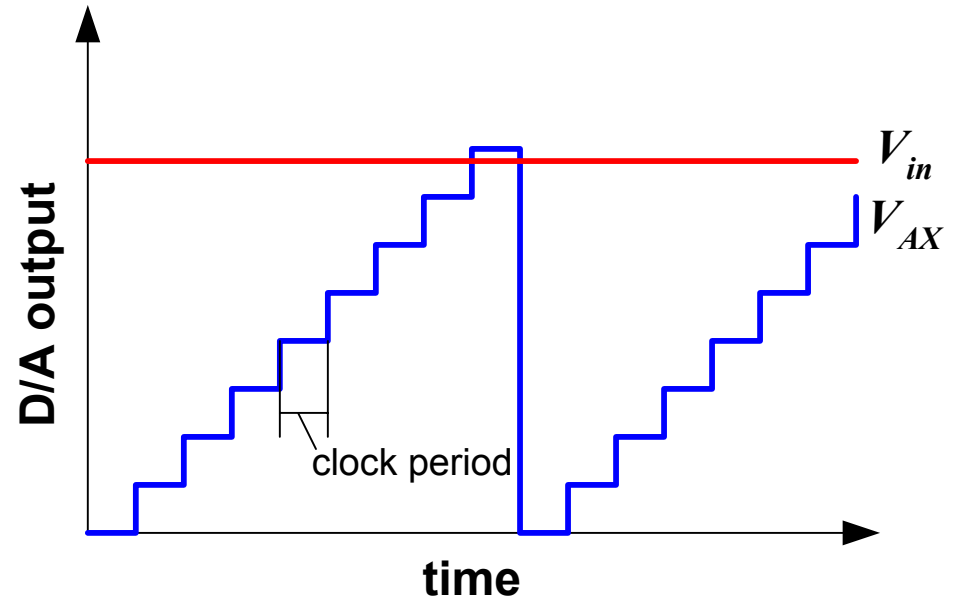
$$T_{C,max} = (2^N - 1) \times \text{Clock period}$$




Successive Approximation Digital Voltmeter

Ex. To determine a number between 0 – 511 (9 bit binary),
given, the number to be determined is 301

No.	Estimate		Results
1	256	1 0000 0000	$V_{in} > V_{AX}$
2	256+128 = 384	1 1 000 0000	<
3	256+64 = 320	1 0 1 00 0000	<
4	256+32 = 288	1 00 1 0 0000	>
5	288+16 = 304	1 00 11 0000	<
6	288+8 = 296	1 00 10 1 000	>
7	296+4 = 300	1 00 10 11 00	>
8	300+2 = 302	1 00 10 111 0	<
9	300+1 = 301	1 00 10 1101	Finished

Successive Approximation Digital Voltmeter

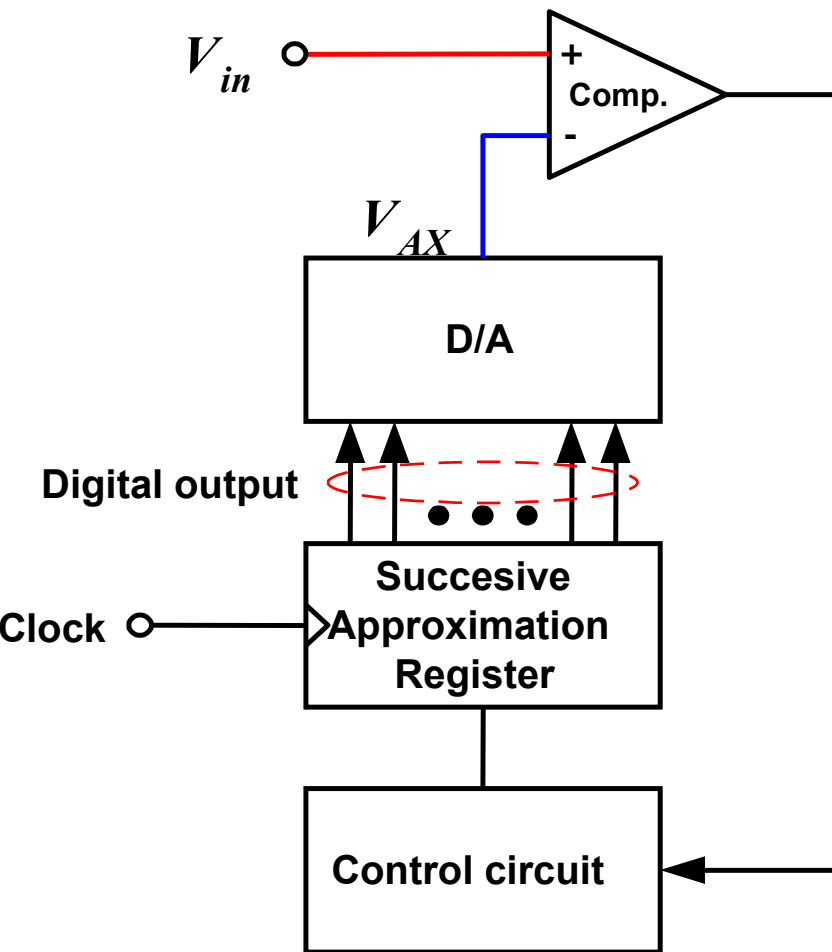Compare the input voltage to the internally generated voltage




Block diagram


- The most common A/D for general applications
- Conversion time is fixed (not depend on the signal magnitude) and relatively fast

$$T_C = N \times \text{Clock period}$$


where N is the number of bits

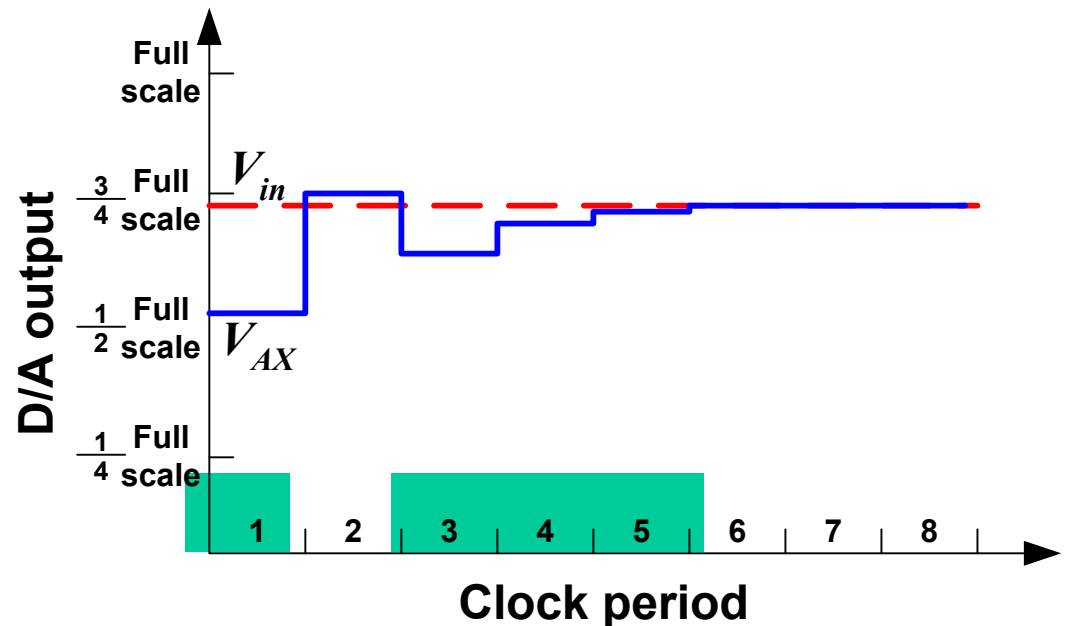

Digital Ramp VS Successive approximation

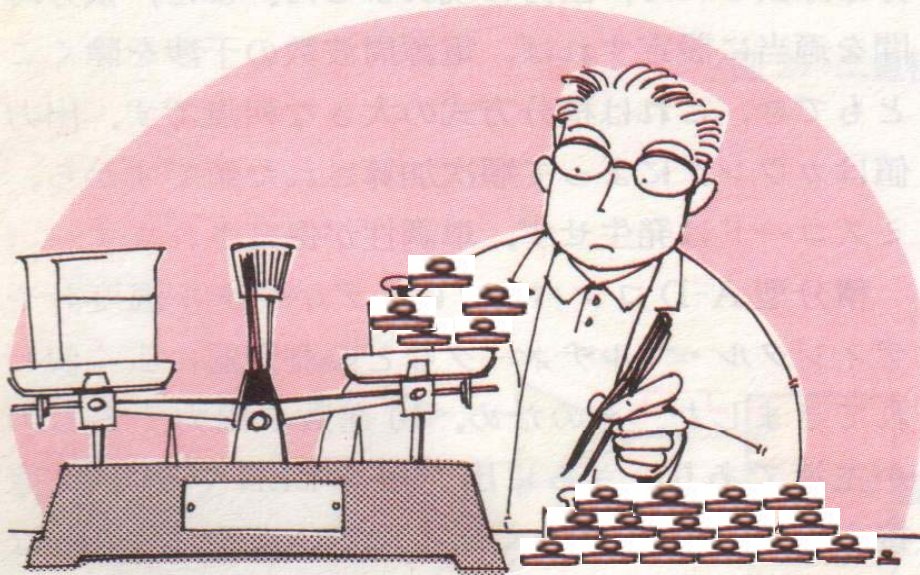


Digital Ramp method

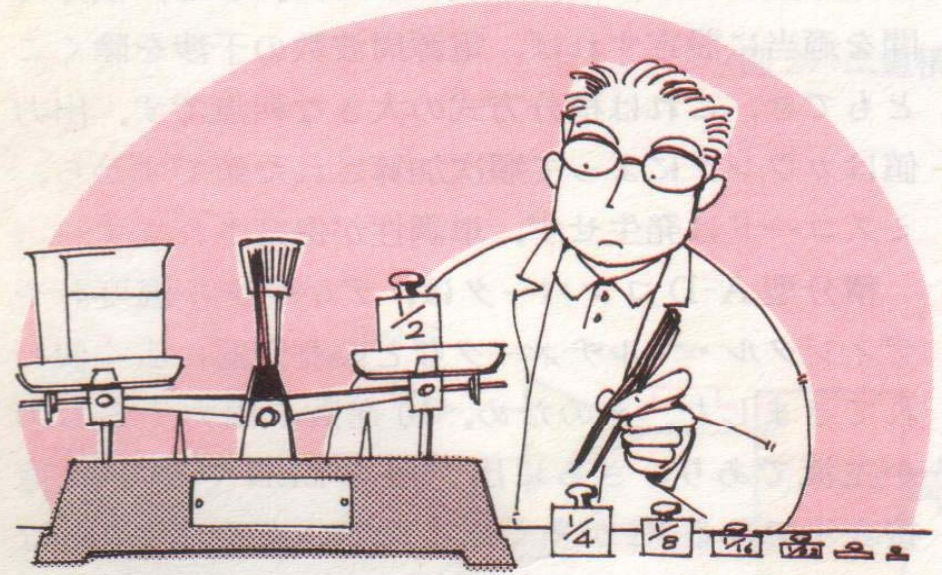

Successive approximation method

Dual-slope Digital Voltmeter


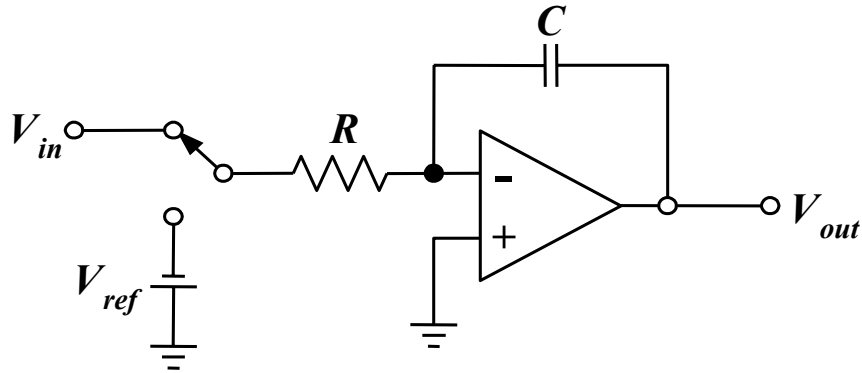


Phase 1: charging C with the unknown input for a given time.

Assume $V_c(0) = 0$

$$V_{out1} = -\frac{V_{in} T}{RC}$$

where T is the charging time

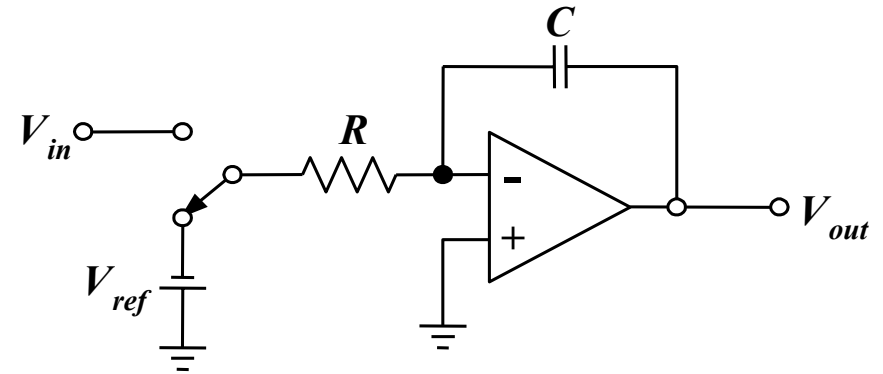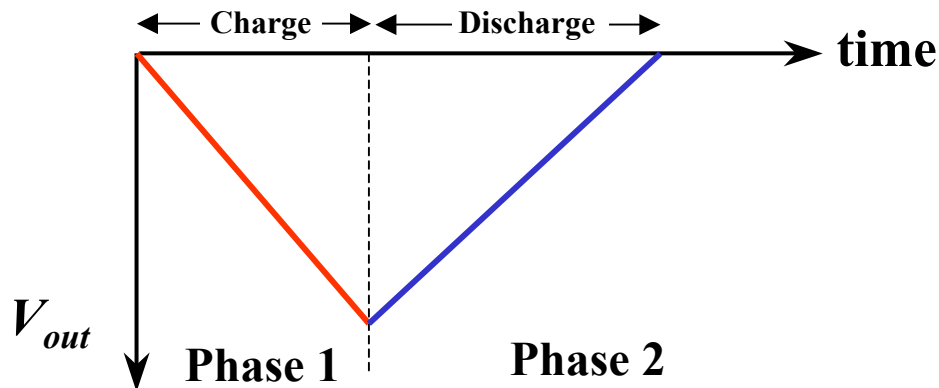


Phase 2: discharging C with the reference voltage until the output voltage goes to zero.

$$V_{out} = \frac{V_{ref} T_x}{RC} + V_{out1}$$


find T_x at which V_{out} becomes zero

$$T_x = \frac{V_{in} T}{V_{ref}}$$

Dual-slope Digital Voltmeter

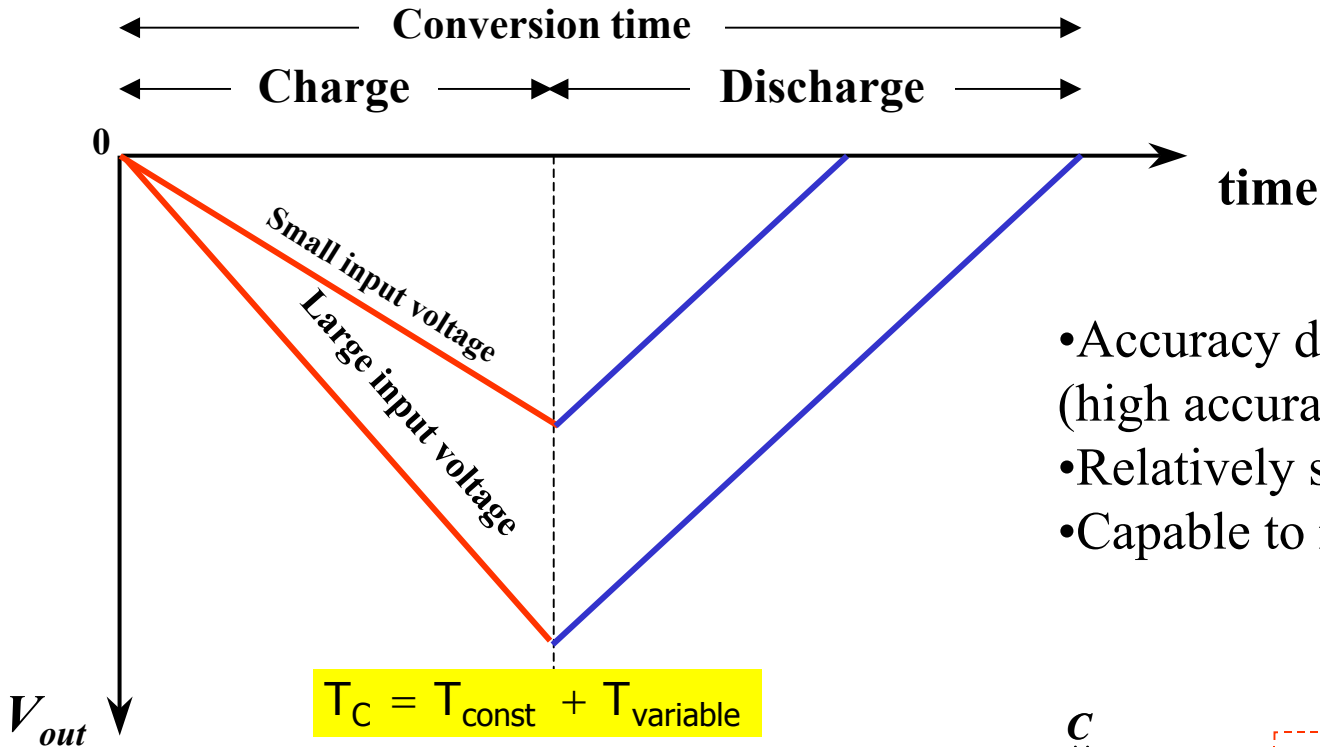

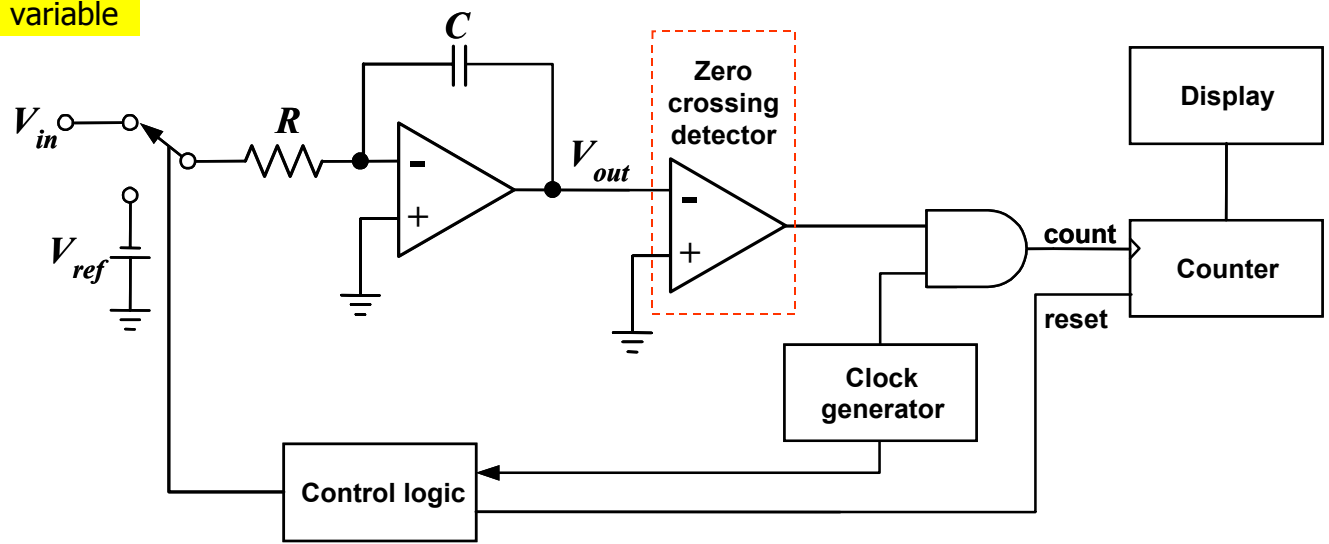- Accuracy does not depend on $R C$ and Clock (high accuracy)
- Relatively slow
- Capable to reject noise



Ex A dual slope A/D has $R = 100 \text{ k}\Omega$ and $C = 0.01 \text{ }\mu\text{F}$. The reference voltage is 10 volts and the fixed integration time is 10 ms. Find the conversion time for a 6.8 volt input.

$$T_x = \frac{V_{in} T}{V_{ref}} = \frac{(6.8 \text{ V})(10 \text{ ms})}{(10 \text{ V})} = 6.8 \text{ ms}$$

The total conversion time is then $10 \text{ ms} + 6.8 \text{ ms} = 16.8 \text{ ms}$

Ans


Ex Find the successive approximation A/D output for a 4-bit converter to a 3.217 volt input if the reference is 5 volts.

- (1) Set $D_3 = 1$ $V_{AX} = 5/2 = 2.5 \text{ Volts}$
 $V_{in} > V_{AX}$ leave $D_3 = 1$
- (2) Set $D_2 = 1$ $V_{AX} = 5/2 + 5/4 = 3.75 \text{ Volts}$
 $V_{in} < V_{AX}$ reset $D_2 = 0$
- (3) Set $D_1 = 1$ $V_{AX} = 5/2 + 5/8 = 3.125 \text{ Volts}$
 $V_{in} > V_{AX}$ leave $D_1 = 1$
- (4) Set $D_0 = 1$ $V_{AX} = 5/2 + 5/8 + 5/16 = 3.4375 \text{ Volts}$
 $V_{in} < V_{AX}$ reset $D_0 = 0$

By this procedure, we find the output is a binary word of 1010_2

Ans

Typical specification of DMM

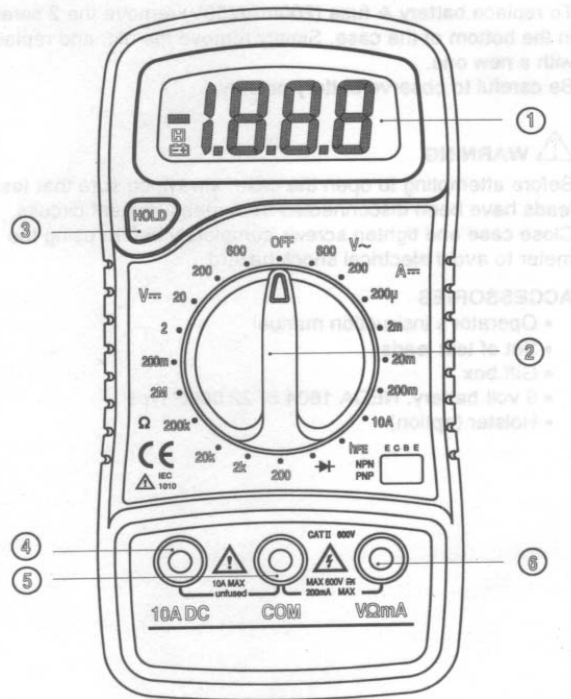

General

Maximum voltage between terminals	:600 V
Fuse protection	:200mA/250V
Power	:9V battery
Display	:LCD 3 1/2 digits, updates 2-3/ sec.
Input impedance	:10 MΩ
Frequency range	:40-400 Hz
Measuring method	Dual-slope integration
Over range indication	Only figure "1" on the display
Polarity indication	"-" displayed for negative polarity

Accuracy of DMM

Indicate as \pm (% of reading + No. of digits)

Ex. \pm (0.5% of rdg + 1 digits) sometimes simplify as \pm (0.5 + 1)

Ex. For an accuracy of \pm (0.5 + 1), calculate the maximum error of in the 1.800 V reading

error = \pm (0.5% of 1.800 + 0.001 V)

= \pm (0.009 + 0.001 V) = \pm 0.01 V or \pm 0.56% of reading

Ex A 20 V dc voltage is measured by analog and digital multimeters. The analog instrument is on its 25 V range , and its specified accuracy is $\pm 2\%$. The digital meter has 3 $\frac{1}{2}$ digit display and an accuracy of $\pm(0.6+1)$. Determine the measurement accuracy in each case.

Analog instrument:

$$\begin{aligned} \text{Voltage error} &= \pm 2\% \text{ of } 25 \text{ V} \\ &= \pm 0.5 \text{ V} \\ \text{error} &= \pm \frac{0.5 \text{ V} \times 100\%}{20 \text{ V}} \\ &= \pm 2.5\% \end{aligned}$$

Digital instrument:

For 20 V displayed on a 3 $\frac{1}{2}$ digit display

$$1 \text{ Digit} = 0.1 \text{ V}$$

$$\begin{aligned} \text{Voltage error} &= \pm (0.6\% \text{ of reading} + 1 \text{ Digit}) \\ &= \pm (1.2 \text{ V} + 0.1 \text{ V}) \\ &= \pm 0.22 \text{ V} \\ \text{error} &= \pm \frac{0.22 \text{ V} \times 100\%}{20 \text{ V}} \\ &= \pm 1.1\% \end{aligned}$$

$\frac{1}{2}$ digit



3 $\frac{1}{2}$ digit display