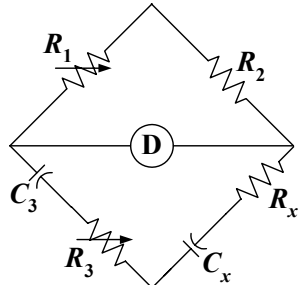
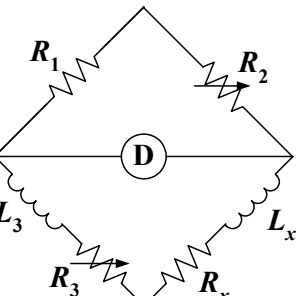
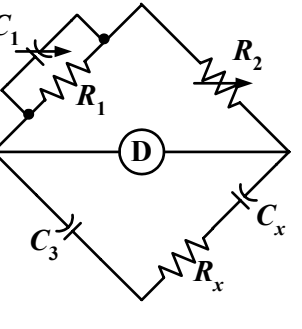
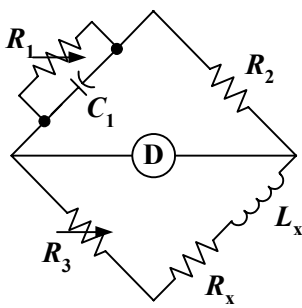
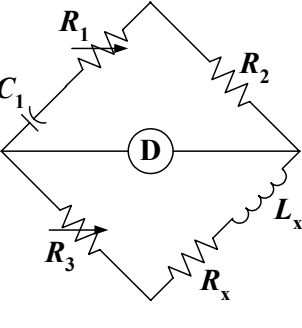
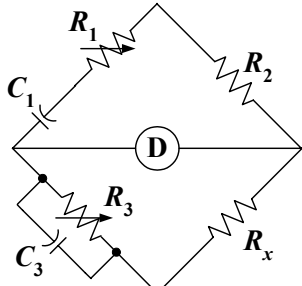


<p><i>Series Capacitance Comparison Bridge</i></p> <p>Most common Capacitance bridge circuit. Usually R_3 and R_1 are variable so that bridge reads capacitance and D</p>		$R_x = R_3 \frac{R_2}{R_1}$ $C_x = C_3 \frac{R_1}{R_2}$ $D = \omega R_3 C_3$
<p><i>Series Inductance Comparison Bridge</i></p> <p>Basic inductance comparison bridge. Additional resistance added to inductor with lower Q to get resistance balance.</p>		$R_x = R_3 \frac{R_2}{R_1}$ $L_x = L_3 \frac{R_2}{R_1}$ $Q = \frac{\omega L_3}{R_3}$
<p><i>Scherring Bridge</i></p> <p>Used in high-voltage bridges with a high voltage capacitor as C_3. Used in high-frequency bridges because variable capacitors can be used for both adjustments. Use in dielectric measurements because C_1 gives high-resolution loss measurement.</p>		$R_x = R_2 \frac{C_1}{C_3}$ $C_x = R_3 \frac{R_1}{R_2}$ $D = \omega R_1 C_1$
<p><i>Maxwell-Wien Bridge</i></p> <p>Most common inductance bridge.</p>		$R_x = \frac{R_2 R_3}{R_1}$ $L_x = R_2 R_3 C_1$ $Q = \omega R_1 C_1$
<p><i>Hay Bridge</i></p> <p>Useful for parallel inductance measurements or high-Q measurements where R_3 of Maxwell bridge would have to be impractically high. Also used for measurements with dc current bias because all current applied across bridge flows in L_x</p>		$R_x \approx \omega^2 C_1^2 R_1 R_2 R_3$ $L_x \approx R_2 R_3 C_1$ <p>for $Q > 10$</p>
<p><i>Wien Bridge</i></p> <p>Useful for determine frequency of a voltage source</p>		$\frac{R_2}{R_4} = \frac{R_1}{R_3} + \frac{C_3}{C_1}$ $f = \frac{1}{2\pi \sqrt{C_1 C_3 R_1 R_3}}$